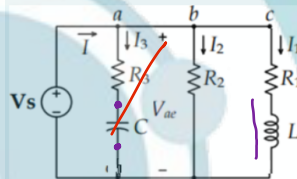


3

According to the figure shown below, which statement is true: ☐

(2 Points)



Assume V_s is DC power supply

capacitor $\rightarrow$ open circuit
inductor $\rightarrow$ short circuit

$$R3 = \frac{2R1}{2} = R1$$

$$V = IR$$

$$I_1 = \frac{V}{2R_2}$$

$$I_2 = \frac{V}{R_2}$$

$$I_1 \text{ is half } I_2$$

☒ Both A and C are correct

☐ Both B and C are correct

☐ B. The current I_1 is double of I_2

☐ D. I_1 is one fourth of I_2

☐ C. $I_3 = 0$


☒ A. The current I_1 is half I_2

$I_3 = 0$
because it becomes open circuit

4

You are asked to connect the following circuit in the lab, to connect it correctly: ☐

(1 Point)

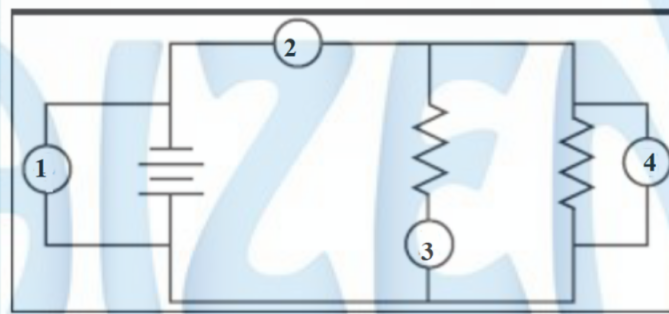

☐ A. Devices 1 and 4 are ammeters, Devices 2 and 3 are voltmeters

☒ B. Devices 2 and 3 are ammeters, Devices 1 and 4 are voltmeters

☐ Both A and C are correct

☐ C. Devices 2 and 4 are ammeters, Devices 1 and 3 are voltmeters


☐ None of these.

Voltmeter parallel

Ammeter series


5

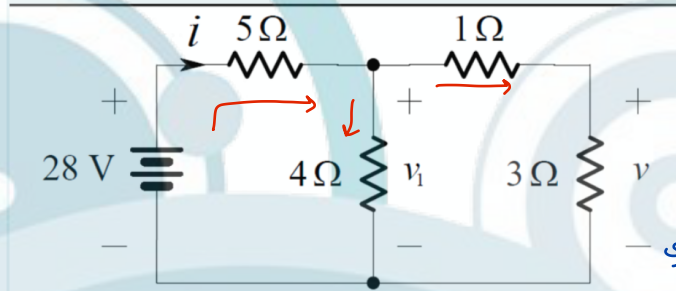According to the figure, which statement is correct: □
(1 Point)



- ☐ None of these
- ☒ C. The current through 4 ohm is equal to the current through 3 ohm
- ☐ A. The voltage across 4 ohm is higher than the voltage across 5 ohm
- ☐ B. The current through 4 ohm is higher than the current through 3 ohm
- ☐ Both A and C


بالمنطق
Series ← 1, 3

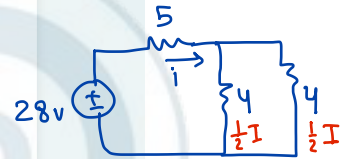

أ سوف يتقسم بشكل متساوي
لأن المقاومة متساوية

6

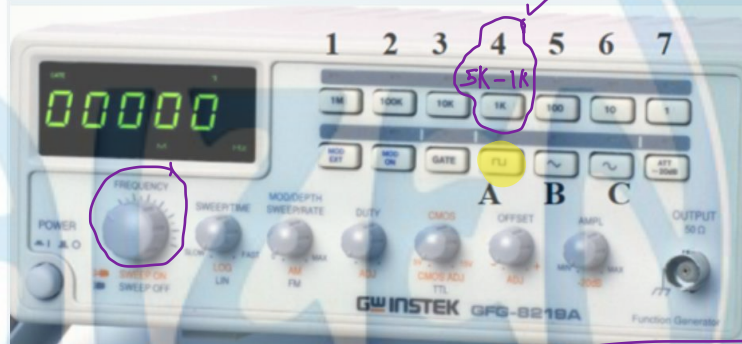For the shown function generator device, if you want to generate a square wave with 3000 Hz, which buttons you have to press: (1 Point)




- ☐ B then 4, then rotate the frequency knob
- ☐ None of the above
- ☐ A then 5, then rotate the frequency knob
- ☐ C then 4, then rotate the frequency knob
- ☒ A then 2, then rotate the frequency knob
- ☐ C then 2, then rotate the frequency knob

A 4 Frequency knob
← هاي صح أكثر لكن لأنها
غير موجودة
بختار من الموجود

ماينفع X

بفعل

7

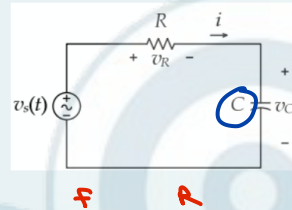

For the series RC circuit shown, given that the source frequency is 150 Hz, $R = 2000 \text{ ohm}$ and the total impedance phase angle is (-75°) degree. The capacitor C value is: (2 Points)


- ☐ 142.2 nF
- ☐ 1.422 nF
- ☐ 14.22 nF
- ☒ 142.2 microF
- ☐ None of the above

$$\begin{aligned} \omega &= 2\pi f \\ &= 2\pi \times 150 \\ \omega &= 300\pi \end{aligned}$$

$$\begin{aligned} -75^\circ &= -\tan^{-1}\left(\frac{1}{\omega CR}\right) \\ \tan(75^\circ) &= \frac{1}{300\pi \times C \times 2000} \\ C &= 1.42 \times 10^{-7} \text{ F} \\ &= 142.15 \text{ nF} \end{aligned}$$

- ☐ None of the above

8

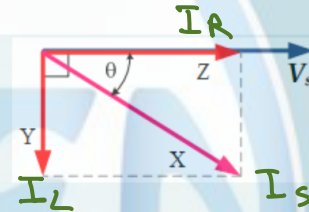

According to the phasor diagram for a parallel RL circuit shown, the symbols X, Y and Z are referred to: (2 Points)

- ☐ X is for inductor current, Y is for source current and Z is for the resistor current
- ☐ X is for resistor current, Y is for source current and Z is for the inductor current
- ☐ X is for source current, Y is for resistor current and Z is for the inductor current
- ☒ X is for source current, Y is for inductor current and Z is for the resistor current
- ☐ None of the above
- ☐ X is for resistor current, Y is for inductor current and Z is for the source current
- ☐ X is for inductor current, Y is for resistor current and Z is for the source current

- ☐ X is for inductor current, Y is for source current and Z is for the resistor current
- ☐ X is for resistor current, Y is for source current and Z is for the inductor current
- ☒ X is for source current, Y is for resistor current and Z is for the inductor current
- ☐ X is for source current, Y is for inductor current and Z is for the resistor current
- ☐ None of the above
- ☐ X is for resistor current, Y is for inductor current and Z is for the source current
- ☐ X is for inductor current, Y is for resistor current and Z is for the source current


9

 V_R

The resistor voltage in a series RL circuit is always out of phase with the source current. ☐

(2 Points)

- ☐ True
- ☒ False

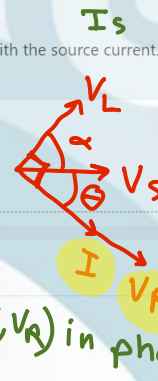

- ☐ A
- ☐ B

11

For a series R-L circuit :

(Note that you can select more than one choice if needed, but the wrong choice will cancel the correct one.)
(2 Points)

- ☐ the inductor impedance is minimum at high frequency
- ☐ None of the above
- ☐ the total impedance Z is totally real
- ☒ the source current is maximum at low frequency
- ☐ the power factor is equal one

$$Z = \frac{V}{I}$$

$$2\pi fL = \frac{V}{I}$$

in (R-L) series


$$I \propto \frac{1}{f}$$

علاقة عكسية



ويشطب

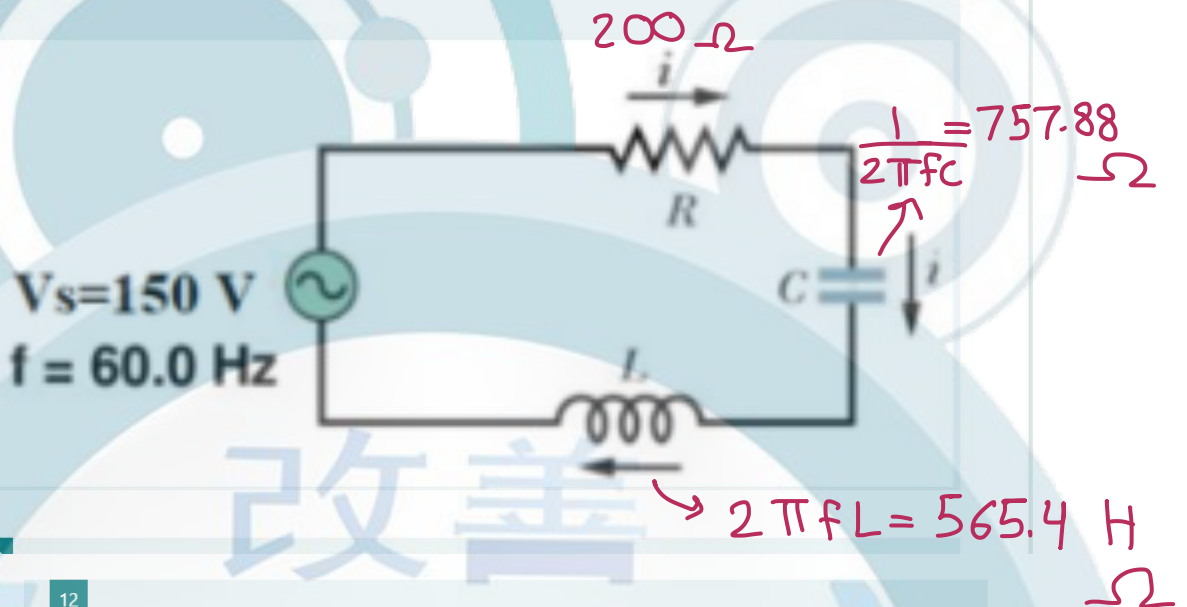For the series R-L-C circuit shown, Given that $R=200\ \Omega$, $L = 1.5\ \text{H}$ and $C = 3.5\ \mu\text{F}$. answer the following questions:



12

The magnitude of total impedance in (ohm) is:
(2 Points)

- ☐ 54.68
- ☐ 303.62
- ☐ None of above
- ☒ 1529.92
- ☐ 1229

1523.36

KAIZER
TEAM

13

The magnitude of the source current is: []
(2 Points)

- ☐ 0.49 A
- ☐ 2.74 A
- ☐ 4.9 A
- ☐ None of above
- ☐ 1.5 A

14

The phase angle between the current and the voltage in (degree) is:
(2 Points)

- ☐ -70.8
- ☐ -43.9
- ☐ -8.72
- ☐ 0.00

15


For a parallel R-L circuit, the correct statement is:
(2 Points)

- ☐ As source frequency decrease, the inductor current will decrease
- ☐ V_s lag I
- ☒ As source frequency increase, X_L increase
- ☐ None of these
- ☐ As source frequency decrease, R will decrease

16

In the case of a parallel R-C circuit, the source current the source voltage.
(2 Points)

- ☒ None of these
- ☐ Leads

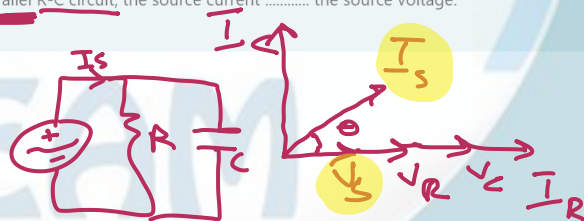


in (R-C)

I_s leads V_s by θ always

17

(R-C) parallel

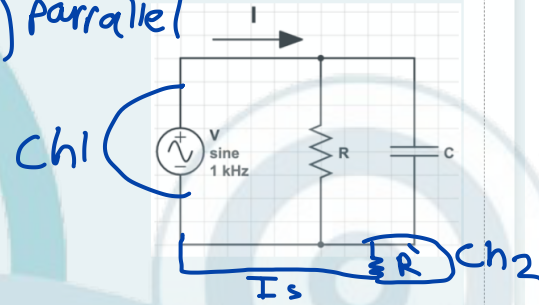

For the circuit shown, if we want to find the phase shift between the source current and the source voltage using the oscilloscope device, then we had to: (2 Points)

- ☒ connect CH1 across V, and connect CH2 in series with V
- ☐ connect CH1 across R, and connect CH2 in series with C
- ☒ An element to the circuit must be added and connect CH2 parallel to it while CH1 is connected to V
- ☐ connect CH1 across V, and connect CH2 across C
- ☐ None of these
- ☐ connect CH1 across V, and connect CH2 across R

18

↓ (R-C) parallel

Frequency ↑

As frequency decreases, which of the following statements is true? (2 Points)


- ☒ both series and parallel RC impedance decrease
- ☐ series RC impedance increases and parallel RC impedance decreases
- ☐ None of these
- ☐ series RC impedance decreases and parallel RC impedance increases
- ☐ both series and parallel RC impedance increase

$X_C \downarrow$ in series
 $X_C \downarrow$ in parallel

in R-C
 (frequency) $\propto \frac{1}{X_C}$
 frequency ↑ $\Rightarrow X_C \downarrow$

TEAM

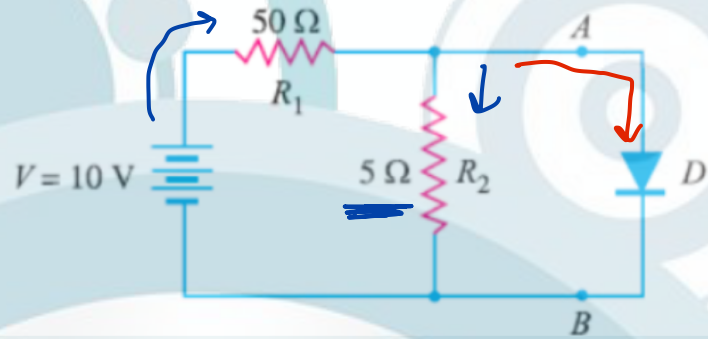Use the figure to answer the following questions, assume practical germanium diode ($V_y = 0.3 \text{ V}$)



19

The voltage (in volt) cross 5 ohm resistor is:
(2 Points)


- ☐ None of above
- ☐ 0.3
- ☐ 0.809
- ☐ 0.909
- ☐ 0.7
- ☐ 0.55

?

KALZEN
TEAM



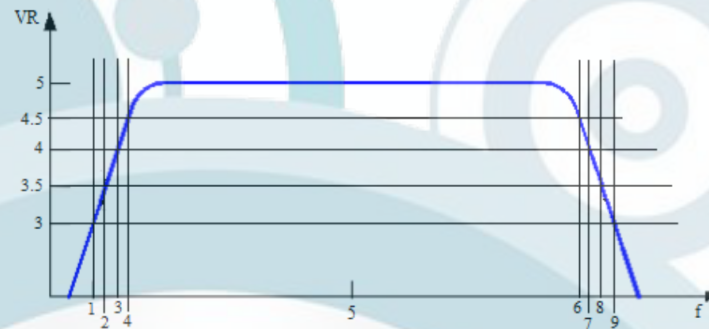For a series R-L-C circuit, the resistor voltage variation with frequency is shown in the figure, answer the following questions:



23

The lower and upper cutoff (corner) frequencies, respectively (f_L and f_H) are: (2 Points)

- ☐ None of the above
- ☐ 4 and 6
- ☒ 2 and 8
- ☐ 1 and 9
- ☐ 3 and 7
- ☐ 5 only

24

The voltage at the resonance frequency is: (1 Point)

- ☐ 3
- ☐ 4.5
- ☐ 5
- ☒ 3.5