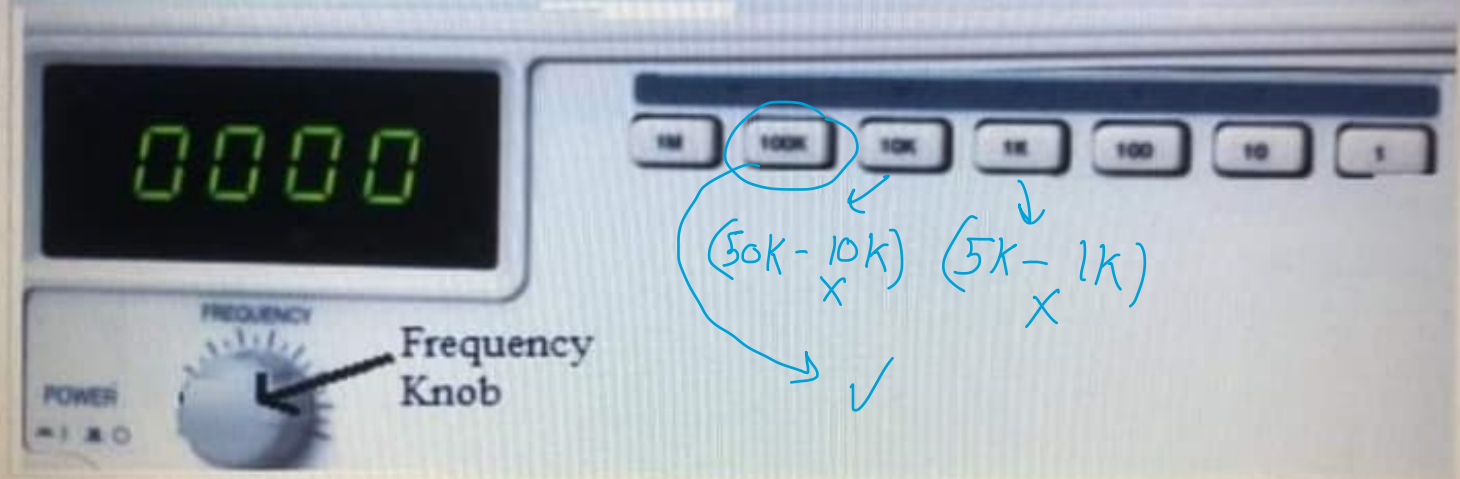


A part of the Function Generator is shown in the Figure, if we want to adjust its output frequency to 90 kHz, we had to:
(1.5 Points)



- ☐ Press the (10) button then rotate the frequency knob
- ☒ Press the (100k) button then rotate the frequency knob
- ☐ Press the (10k) button then rotate the frequency knob
- ☐ Press the (100) button then rotate the frequency knob

5

If a resistor has the following colors (Orange, White, Red, and gold) then the range value of this resistor is:
(1.5 Points)


- ☒ None of the above
- ☐ 3270Ω ± 40% (400Ω)
- ☐ 3270Ω ± 40% (400Ω)
- ☐ 3270Ω ± 40% (400Ω)



A student connects the following circuit with three current sources ($I_1 = 3\text{ A}$, $I_2 = 4\text{ A}$ and $I_3 = 6\text{ A}$) and he added two Ammeters (A1 and A2) and one voltmeter (V).

The reading of the ammeter A2 (in A) will be:

(2 Points)

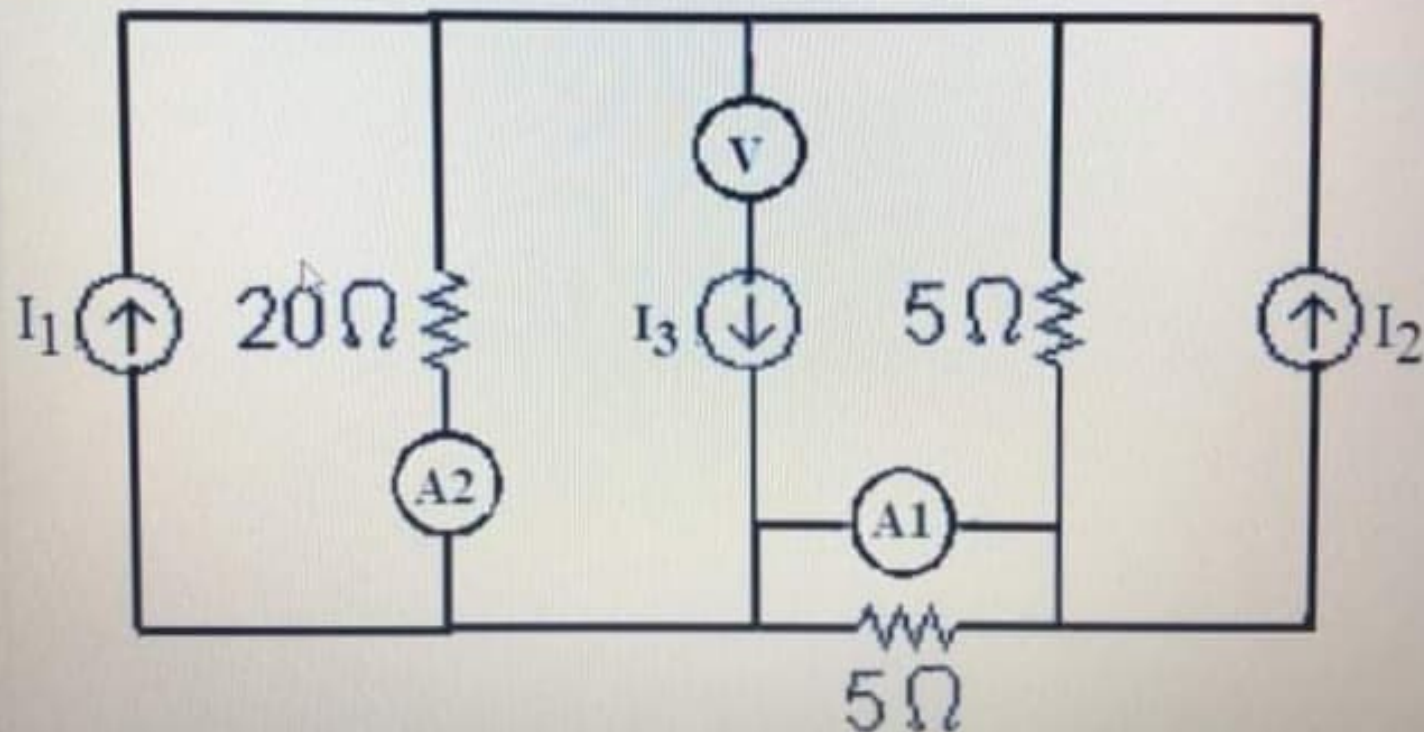

6

• BLACK: 0	• GREEN: 5
• BROWN: 1	• BLUE: 6
• RED: 2	• VIOLET: 7
• ORANGE: 3	• GREY: 8
• YELLOW: 4	• WHITE: 9

Use the following table to calculate the value of the resistor that has colors (White, Green, Red, and Silver) while the Silver color represents 10% tolerance.

The maximum value of the resistor will be:
(2 Points)

+

$$95 \times 10^2 \pm .1$$

$$9500 \pm (0.1 \times 9500)$$

$$= 10450 \Omega$$

Enter your answer

In the oscilloscope device, the knob that determines number of the displayed signal cycles on the screen is :

(1.5 Points)


- ☐ Vertical position
- ☒ Time per Div
- ☐ Horizontal position
- ☐ Volt per Div

عدد ال cycles


$f = \frac{1}{T}$ ← frequency يعني



(Time per Div)

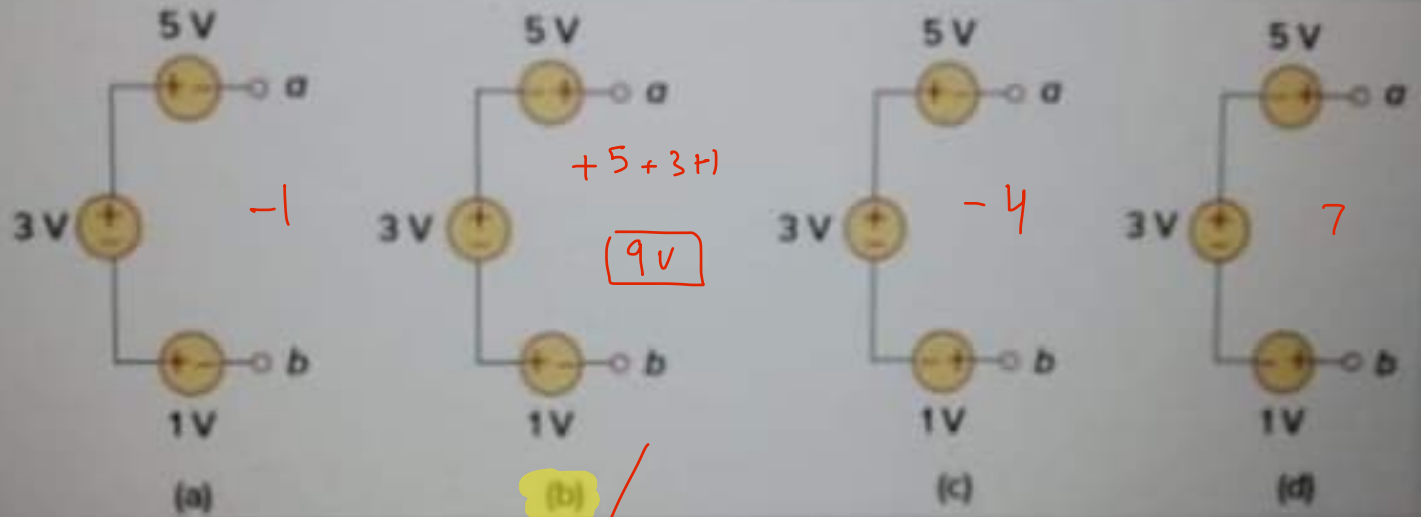The circuit that give $V_{ab} = 9V$ is
(1.5 نقطة)



$V_{ab} = 9V$
من b إلى a

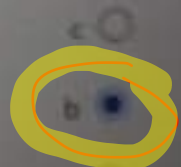

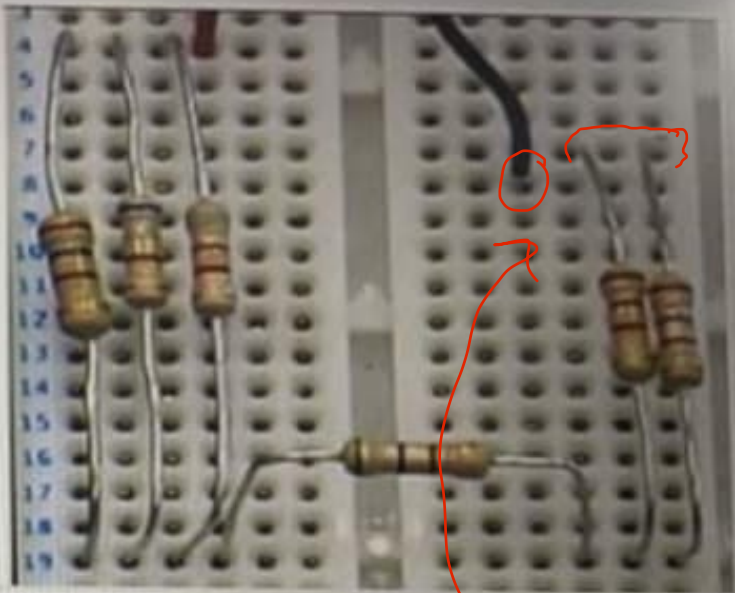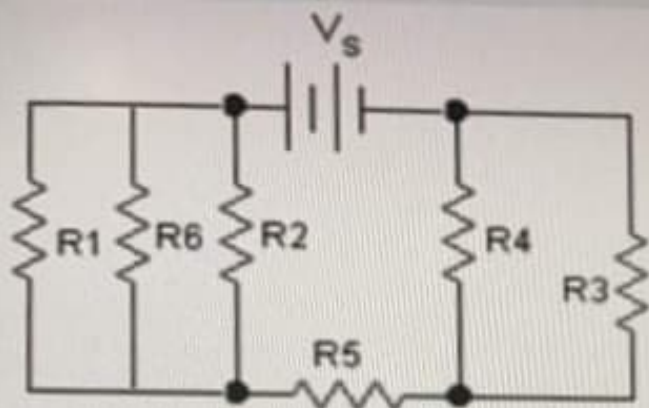

4

Is the shown circuit built correctly?
(2 Points)

☒ Yes


حسب ما اری
انه مو نفس ال Node
فاذا غلط

لكن اذا طلعت نفس ال Node
یعنی صح

Applying Norton's theorems to a circuit yields to: 

(1 Point)

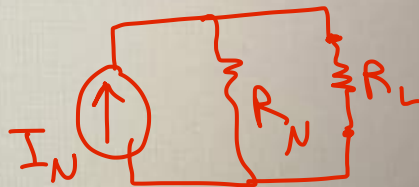- ☐ equivalent voltage source and a resistor in series
- ☒ equivalent current source and a resistor in parallel
- ☐ equivalent current source and a resistor in series
- ☐ equivalent voltage source and a resistor in parallel





4


To measure the voltage across an element in any circuit:
(2 Points)

- ☐ You need a voltmeter connected in series with the element
- ☐ You need an ammeter connected in parallel with the element
- ☒ You need a voltmeter connected in parallel with the element
- ☐ You need an ammeter connected in series with the element


نکته

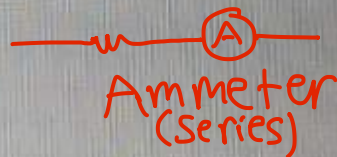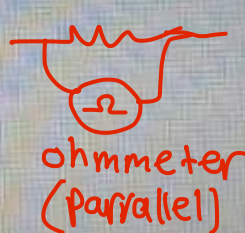

5

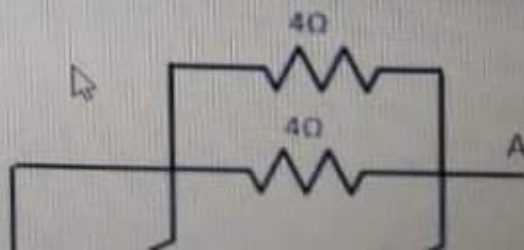

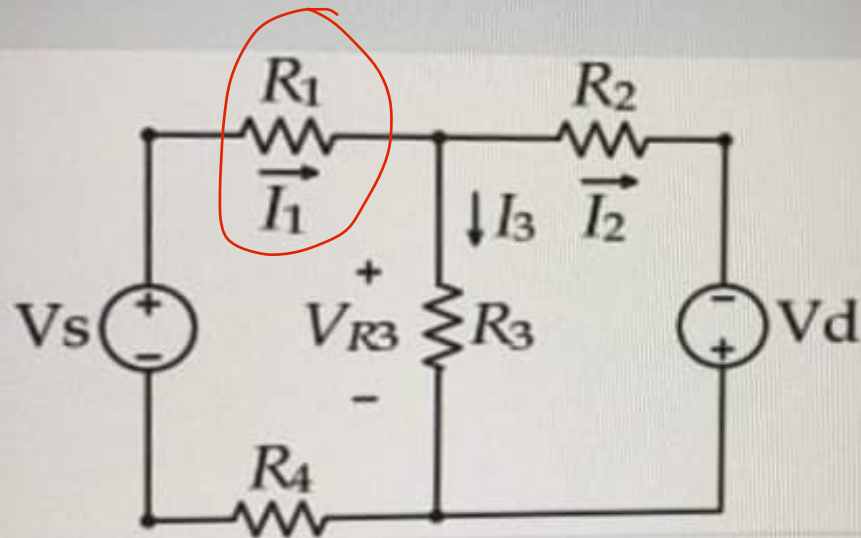The circuit shown below is experimentally conducted by applying the superposition method for the circuit currents, where the results are presented in the table as shown (in ampere). Accordingly, please answer the following:



	Due to V_s only	Due to V_d only
I_1	8.19	4.49
I_2	2.62	-4.01
I_3	5.57	8.5

$$I_1 = 8.19 + 4.49 = 12.68$$

11

The total absorbed power by $R_1 = 390 \text{ ohm}$ (in kWatt) is:

(2 Points)

$$P = I^2 R = 12.68^2 \times 390 = 62.705 \text{ KW}$$

The total absorbed power by $R_1 = 390 \text{ ohm}$ (in kWatt) is:
(2 Points)

$$I_{\text{total}} = 8.19 + 4.49 = 12.68$$

$$\begin{aligned} P_{R_1} &= R I^2 \\ &= 390 \times (12.68)^2 \\ &= 62705.136 \text{ W} \\ &= 62.705 \text{ kW} \end{aligned}$$

62.705

12

The voltage drop on $R_3 = 40 \text{ ohm}$ (in volt) due to both supplies is:
(2 Points)

$$I_{\text{total } 3} = 5.57 + 8.5 = 14.07 \text{ A}$$

562.8


$$\begin{aligned} V_{R_3} &= I_3 R \\ &= 14.07 \times 40 \\ &= 562.8 \end{aligned}$$

13

IF $R_1 = 7 \text{ ohm}$, $R_4 = 8 \text{ ohm}$ and $R_3 = 30 \text{ ohm}$, then the value of the resistor R_2 (in ohm) for power transfer is:

Referring to the signals shown on the scope screen above, if both signals have frequency 4KHz while the CH1 scale = 0.85 volt/Div. Answer the following questions:

یعنی vertical

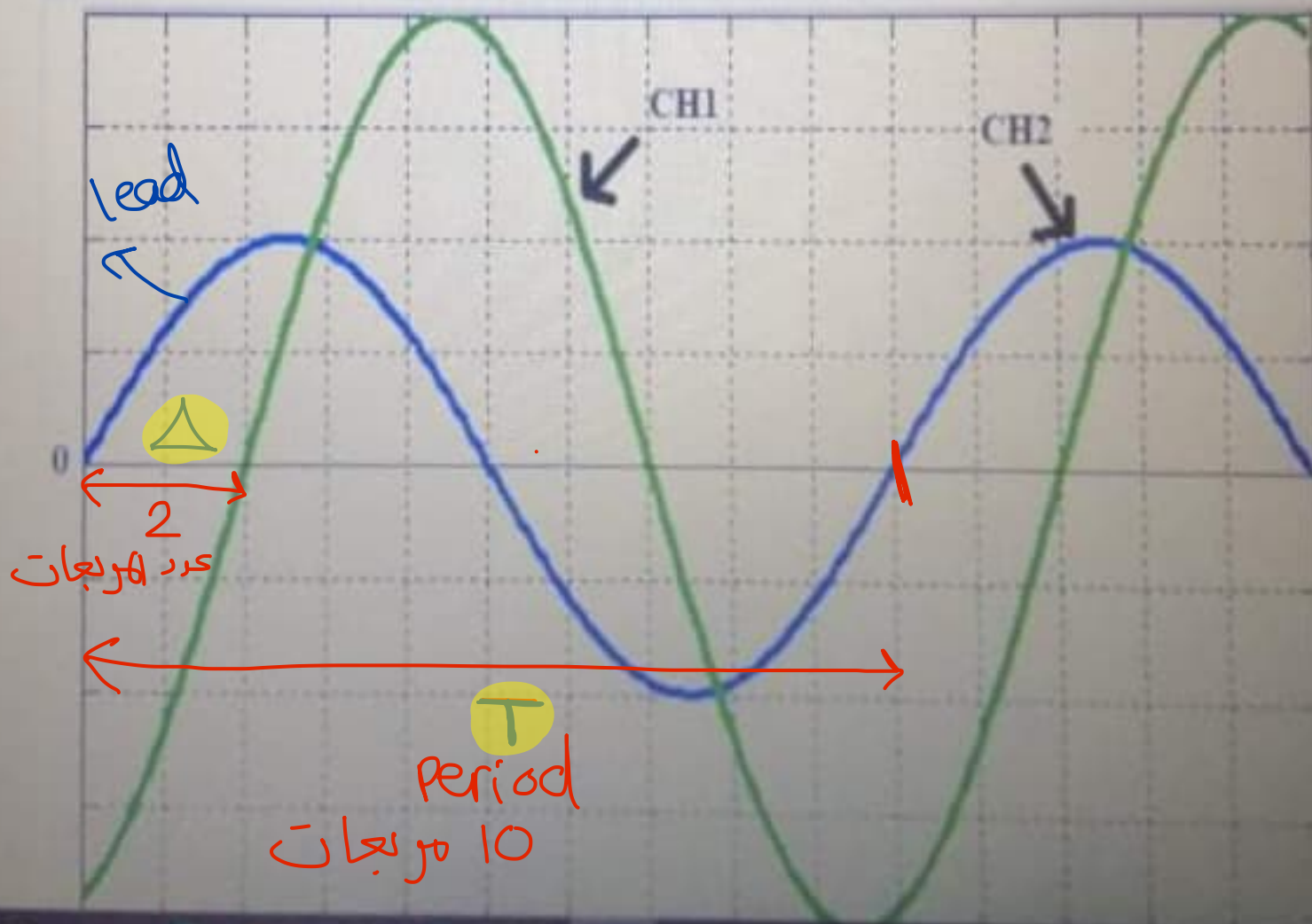

20

CH2 lead CH1 .
(1 Point)

- ☒ True
- ☐ False
- ☐ Can't be determined

21

The phase angle (in degree) between the two signals is:
(2 Points)

$$\theta = \frac{\Delta \times 360^\circ}{T} = \frac{2 \times 360}{10} = 72^\circ$$


4

To measure the current passing through an element in any circuit: [5]
(2 Points)

- ☐ You need an ammeter connected in parallel with the element
- ☐ You need a voltmeter connected in series with the element
- ☐ You need a voltmeter connected in parallel with the element
- ☐ You need an ohmmeter connected in series with the element
- ☐ You need an ohmmeter connected in parallel with the element
- ☒ You need an ammeter connected in series with the element

Ammeter connected series

5

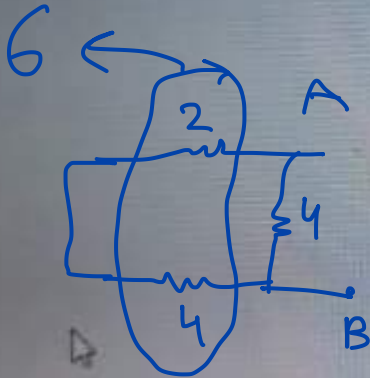


$$6 \parallel 4 = 2.4$$

 R_{th}

حذروا لأن في
هنا سلك فاني
عالتوازي

Kill
all sources
حبيّر
short
circuit

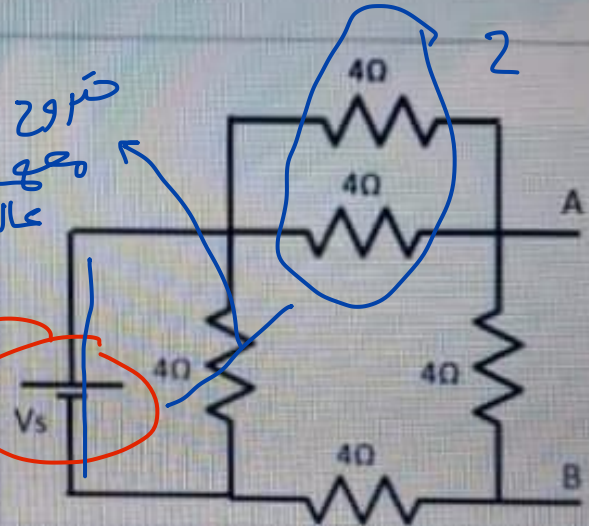

For the following circuit, the Thevenin resistance between A and B (in ohm) is

(2 Points)

$$R_{th} = 2.4$$

Enter your answer


5

For the circuit shown, if the resistor $R = (\text{Orange, Violet, Brown, Brown, Silver})$, then the equivalent resistance (in ohm) between the terminals a and b is (ignore the tolerance):
(2 Points)

3 7 1 $\times 10^1 \pm 1$ ignore tolerance

3710

Black	0	Blue	6
Brown	1	Violet	7
Red	2	Grey	8
Orange	3	White	9
Yellow	4	Gold	$\pm 5\%$
Green	5	Silver	$\pm 10\%$

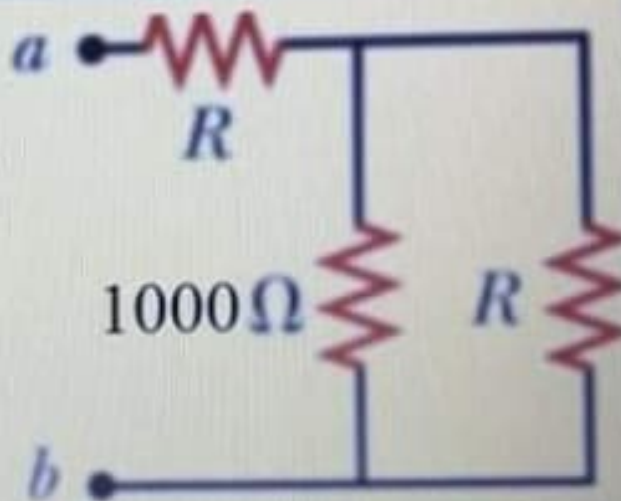

Enter your answer


3710 Ω

Back

Next

Page 2 of 9

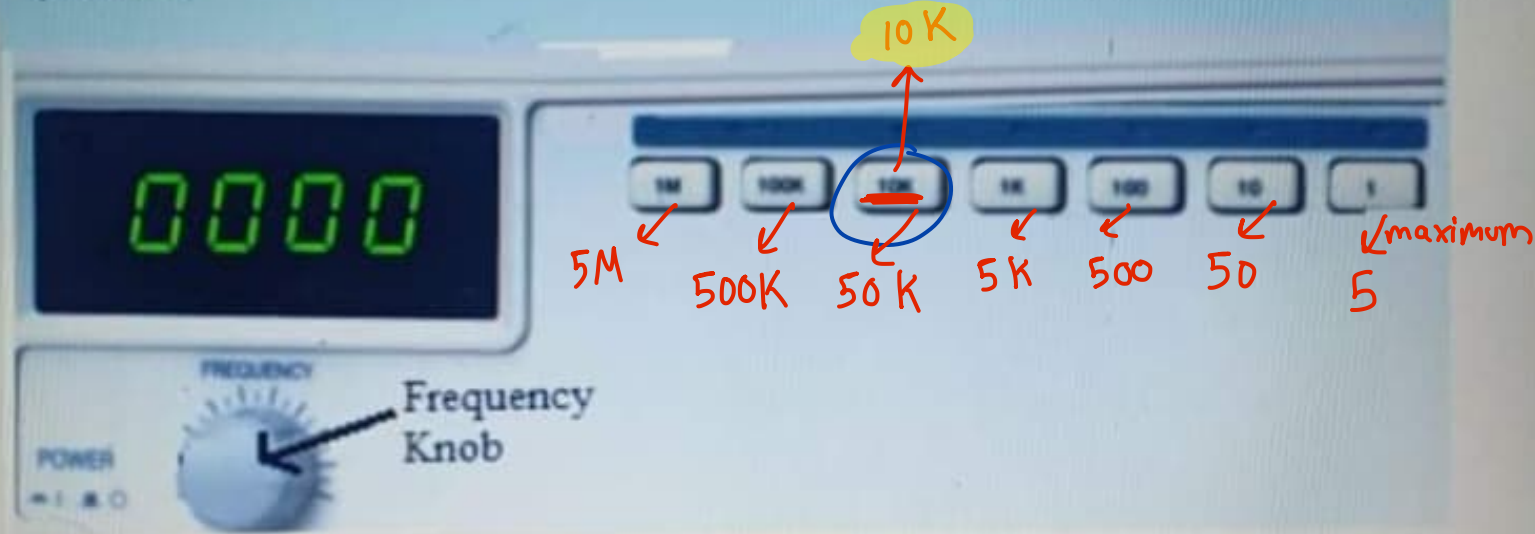A part of the Function Generator is shown in the Figure, if we want to adjust its output frequency to 9 kHz, we had to:
(1.5 Points)



- ☐ Press the (100k) button then rotate the frequency knob
- ☐ Press the (100) button then rotate the frequency knob
- ☐ Press the (10) button then rotate the frequency knob
- ☒ Press the (10k) button then rotate the frequency knob

13

In the oscilloscope, the volt/div knob controls:
(1.5 Points)

- ☐ The number of time for each horizontal division on the screen.
- ☐ The number of time for each vertical division on the screen.
- ☒ The number of volts for each vertical division on the screen.
- ☐ The number of volts for each horizontal division on the screen.

Back

Next

Page 8 of 19

This content is created by the owner of the form. The data you submit will be sent to the form owner. I privacy or security practices of its customers, including those of this form owner. Never give out your p

Powered by Microsoft Forms | Privacy and cookies | Terms of use


The correct connection and reading in the following Figure is:

فاد الجهاز فقط بقراءة

(1.5 Points)

متش متأكدة، بس اظن ه

components → Resistor
Inductor
Capacitor

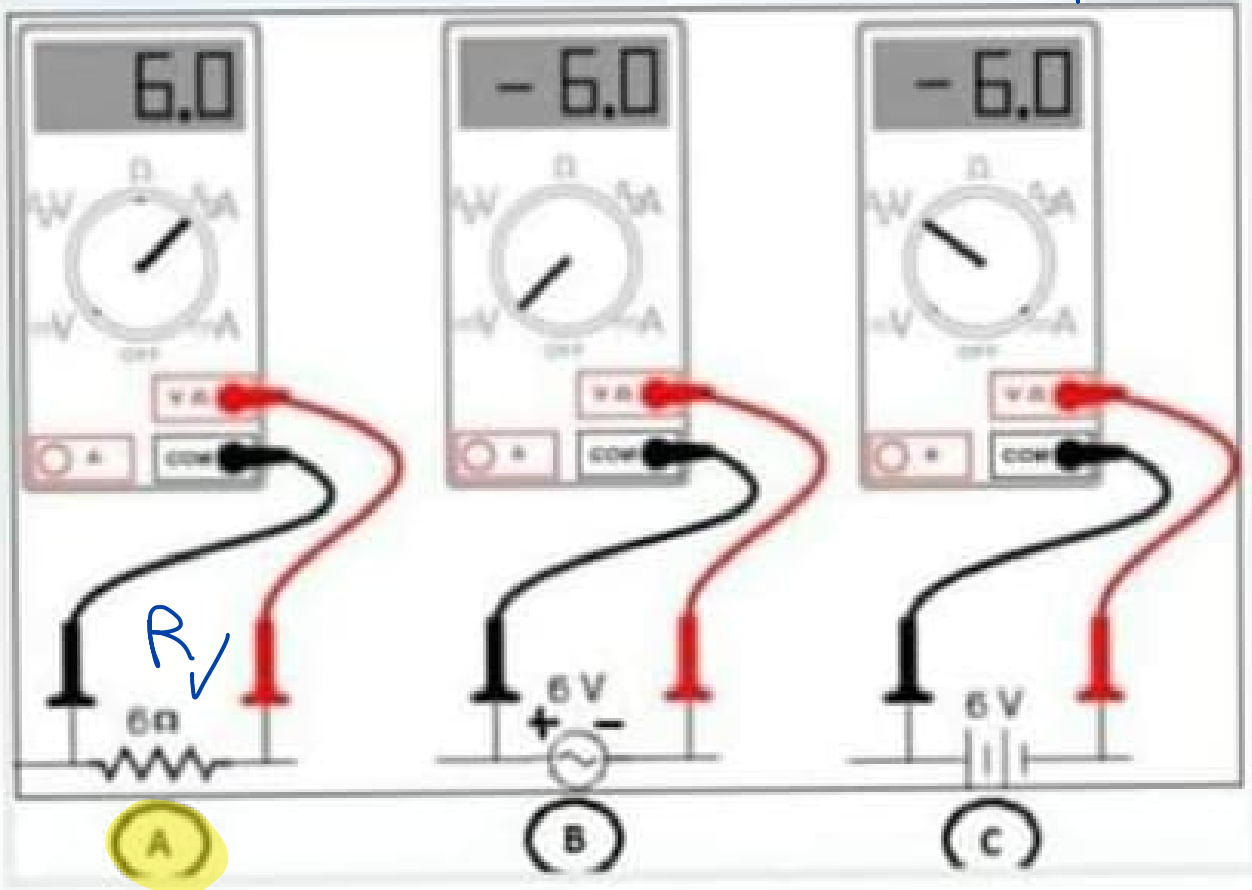

☒ A



☐ B

☐ C

☐ None is correct

in DC $\text{---} \text{||} \text{---}$ capacitor $\rightarrow$ open circuit

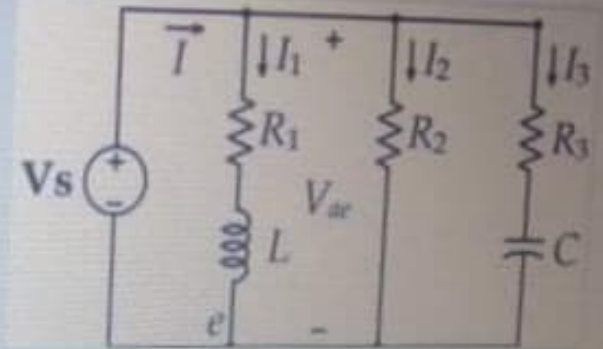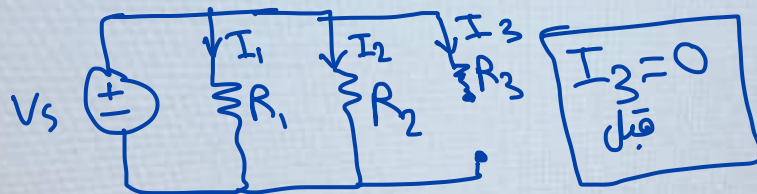$\text{---} \text{---} \text{---}$ inductor $\rightarrow$ short circuit



Replacing the capacitor (C) (in the circuit shown next) by an inductor will: (2 Points)

- ☐ increase the value of the current (2)
- ☐ decrease the value of the total current (1)
- ☒ increase the value of the total current (1)
- ☐ make no changes to the total current (1)
- ☐ make the current (I1) equal to zero

↓ راح يصير short circuit
↓ راح يدخل R3 بالمولد
كأن Req حصل لانه توازي

$$V = I R$$


↑ راح يـ ↓ راح يقل

☆
من متأكد

A student connected the circuit shown and he measured the resistor voltages and recorded them in the shown table (in volt), but accidentally he wrote one of the readings wrong. The wrong voltage (V1 or V2 or V3) is:
(2 Points)

توازي دانا' لازم نفس الجهد
V1 و V3

V1	V2	V3
10	-20	-10

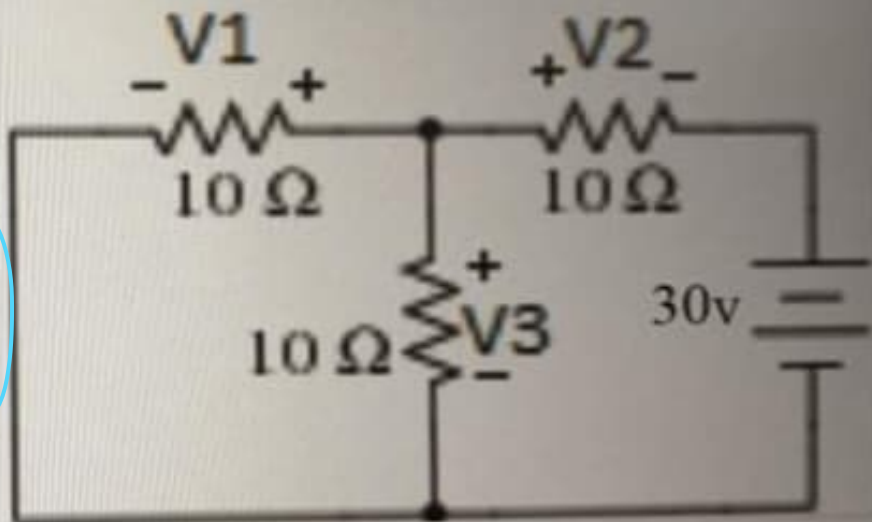

14

Applying Thevenin's theorems to a circuit yields to:
(1 Point)

→ equivalent voltage source and a resistor in series

☒ equivalent voltage source and a resistor in series

☐ equivalent voltage source and a resistor in parallel

☐ equivalent current source and a resistor in series

☐ equivalent current source and a resistor in parallel



15

To find the Norton resistor of a circuit, we had to open all the current sources and short all the voltage sources.
(1.5 Points)

☐ True

☐ False



20/2

100%

100%

6. In a series RC circuit, 12 V(rms) is measured across the resistor and 15 V(rms) is measured across the source voltage, the capacitor peak voltage (in volt) is:

(1.5 Points)

ماری

☐ 9

☒ 12.73

☐ 26


☐ None of above

Back

Next



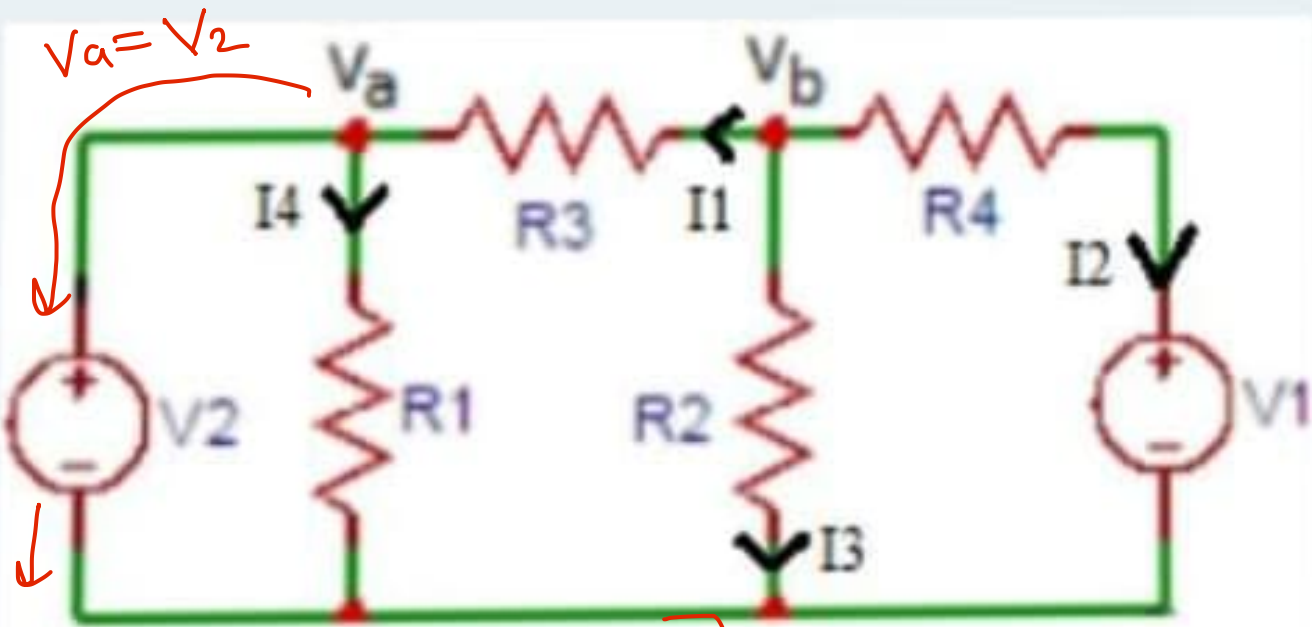A student wrote the Nodal equation at node (b) for the circuit shown here (as shown below it), the missing term in the box is:
(1 Point)



$$\frac{V_b}{R2} + \frac{V_b - V_1}{R4} + \boxed{\frac{V_b - V_a}{R3}} = 0$$



$V_a = V_2$

☐ $(V_b + V_2) / R3$

$\frac{V_b - V_2}{R3}$

☒ $(V_b + V_1) / R4$

For the following circuit, the equivalent
 * resistance (in ohm) is
 (1 نقطة)

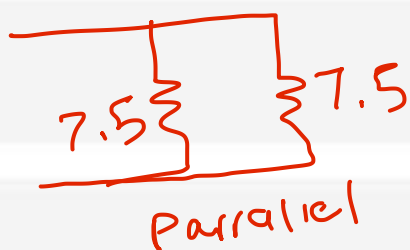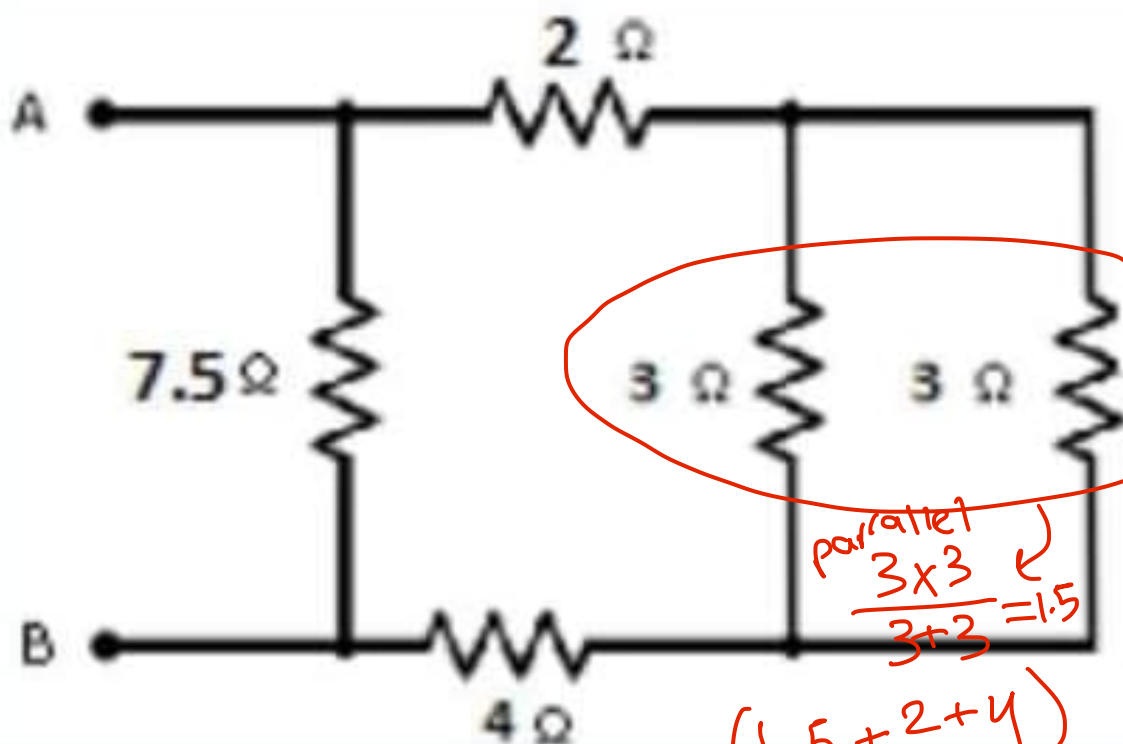1.6 ☐2.6 ☐3.75 ☒None of the above ☐

10

A resistor has a nominal value of ($R=4700$) ohm, and a measured value using an ohmmeter is 4230 ohm. The expected color code for this resistor is: 
(1.5 Points)

- ☐ yellow, violet, red and gold
- ☐ yellow, violet, red and silver
- ☒ yellow, violet, orange and silver
- ☐ yellow, violet, red

Back


Next

Page 3 of 3

The voltage (V) on the 4 ohm resistor (in volt) is:
(2 Points)

DC

$6V$ $\frac{6}{2+4} = 1A$

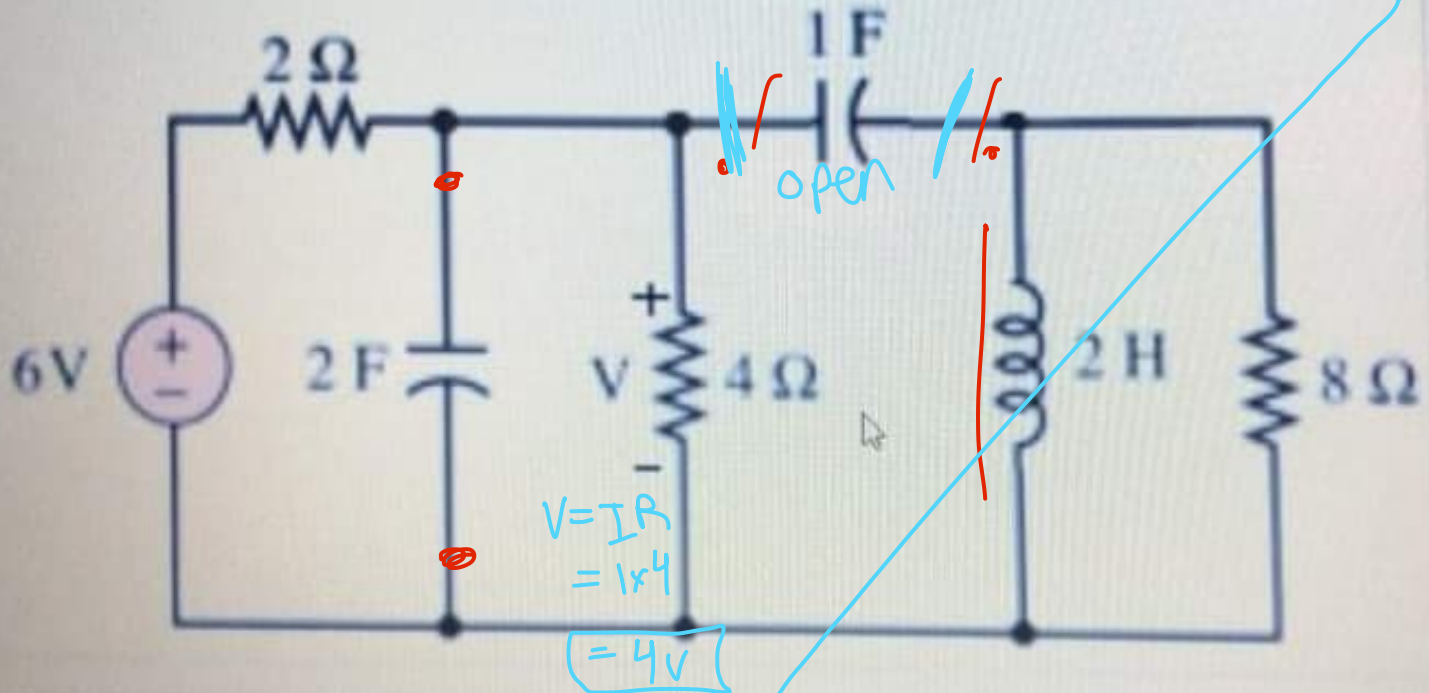

$V = IR$
 $= 1 \times 4$
 $= 4V$

Enter your answer: $= 4 V$

Back

Submit

15

$$R_N = R_{th}$$

To find the Norton resistor of a circuit, we had to short all the current sources and open all the voltage sources. 
(1.5 Points)

خطأ لازم العكس
current source $\rightarrow$ open circuit
voltage source $\rightarrow$ short circuit

☐ True

☒ False

Back

Next

Page 7 of 9

7. If the value of R in a series RLC circuit is increased, then the resonant frequency will:
(1.5 Points)

بیست و یک
11

☐ Increases

☐ decreases

☐ be reduced to zero

☒ not affected

8. If the resistance value is doubled in a series RL circuit, then the magnitude of the total impedance of a circuit will:
(1.5 Points)

$$Z = R + X_L$$

↑ ↑
تزداد ↑

☒ increased

☐ decreased

☐ fixed


☐ Can't be determined without valuse

For the shown function generator, if you want to generate a square wave with 7500 Hz, which buttons you have to press?

(1 Point)



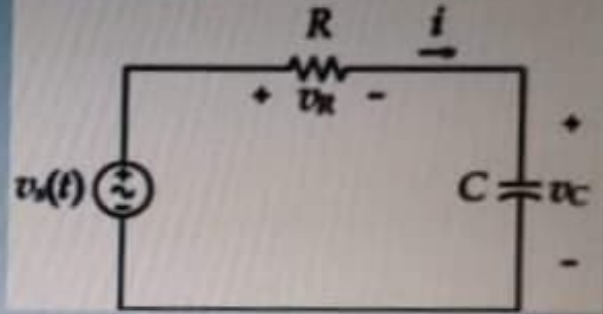- ☒ A then 3, then rotate the frequency knob
- ☐ 5 then 3, then rotate the frequency knob
- ☐ C then 3, then rotate the frequency knob



$$\omega = 2\pi f = 300\pi$$

For the shown series RC circuit, the source frequency is 150 Hz, $R = 2000$ ohm and the phase angle of the total impedance is (-75°) degree. The capacitor C value is:
(2 Points)

☐ 14.22 nF

☒ 142.2 nF

☐ 1.422 nF

☐ None of the above


☐ 142.2 microF

$$\angle Z = -\tan^{-1}\left(\frac{1}{\omega R C}\right)$$

$$-75^\circ = -\tan^{-1}\left(\frac{1}{300\pi \times 2000 \times C}\right)$$


$$\tan(75^\circ) = \frac{1}{300\pi \times 2000 \times C}$$

$$C = 142.15 \text{ nF}$$

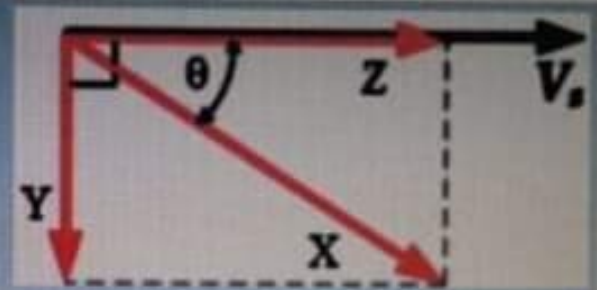

According to the shown phasor diagram of a parallel RL circuit, the symbols X, Y and Z refer to: 
(2 Points)

- ☐ None of the above
- ☐ X is for source current, Y is for resistor current and Z is for the inductor current
- ☐ X is for resistor current, Y is for source current and Z is for the inductor current
- ☐ X is for inductor current, Y is for resistor current and Z is for the source current
- ☐ X is for resistor current, Y is for inductor current and Z is for the source current
- ☒ X is for source current, Y is for inductor current and Z is for the resistor current
- ☐ X is for inductor current, Y is for source current and Z is for the resistor current

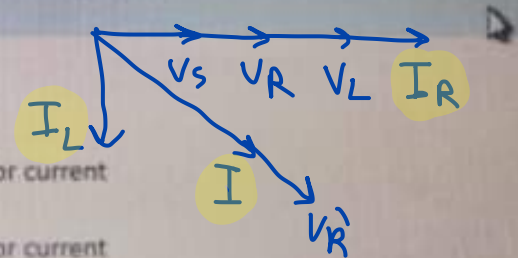

8

For a series RL circuit : 
(2 Points)

R-L series

frequency $\frac{1}{\omega}$ I_s
($\hat{I}_{ms}$ $\hat{I}_{rms}$)

- ☐ None of the above
- ☐ the power factor is equal one
- ☐ the inductor impedance is low at high frequencies
- ☒ the source current is high at low frequencies
- ☐ the total impedance Z is totally real

15
In the case of a parallel RC circuit, the source current ^{I_s} _____ the source voltage. ^{V_s}
(2 Points)

☒ Leads

☐ None of these



☐ Lags

☐ Remains in phase with


in RC
(I_s) leads (V_s) by θ always

If the diode is working well, which of the following represents a correct reading?
(A or B or C)


(2 Points)

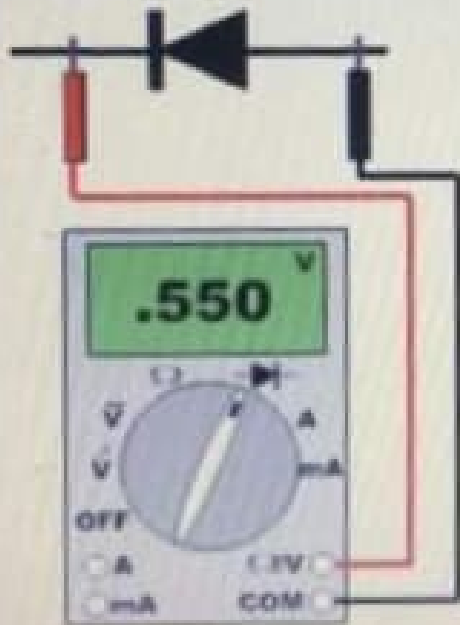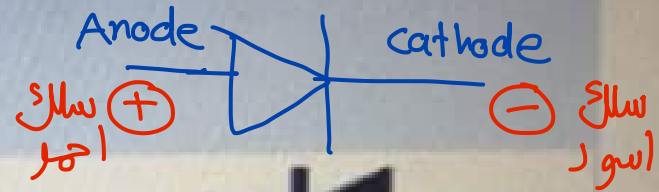

(A)

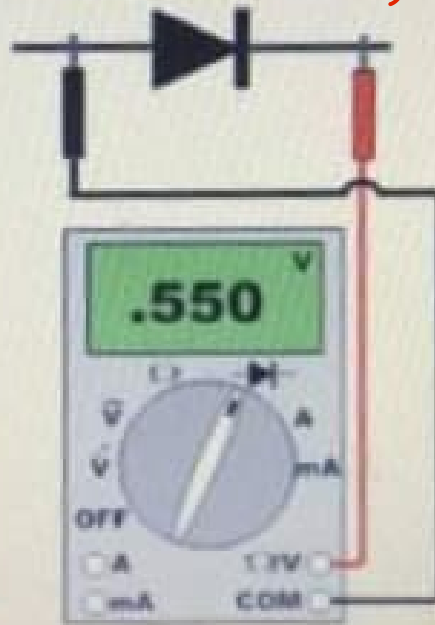

(B)

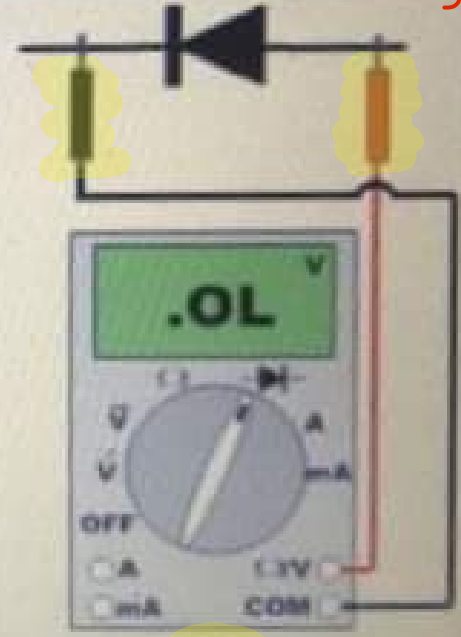

(C)

☐ None of the above

اضمن ملغي

If a supply voltage with 4 Vrms is input to a Full Wave Rectifier circuit, then the output rectified voltage will be (all diodes voltage have $V_f = 0.7$ V): 
(2 Points)

- ☐ 3.3 V
- ☒ None of the above
- ☐ 1.43 V
- ☐ 2.82 V
- ☐ 2.13 V
- ☐ 2.6 V
- ☐ 4.26V



The signal A is the output of : ☐

(1 Point)

- ☐ half wave rectifier circuit
- ☒ full wave rectifier circuit
- ☐ resonance circuit
- ☐ damper circuit
- ☐ clipper circuit
- ☐ none of these

We could achieve the signal B by:
(1 Point)


- ☐ connecting a resistor on the output
- ☒ connecting a capacitor on the output
- ☐ removing a capacitor from the output
- ☐ add a diode
- ☐ removing a resistor from the output
- ☐ add an inductor
- ☐ add potentiometer

If the frequency of the input waveform signal is 100 Hz, then the frequency of the signal A is:
(1 Point)

- ☐ Can't be determined because it is not sinusoidal
- ☒ 100 Hz
- ☐ 50 Hz
- ☐ 200 Hz
- ☐ 0
- ☐ None of these

?

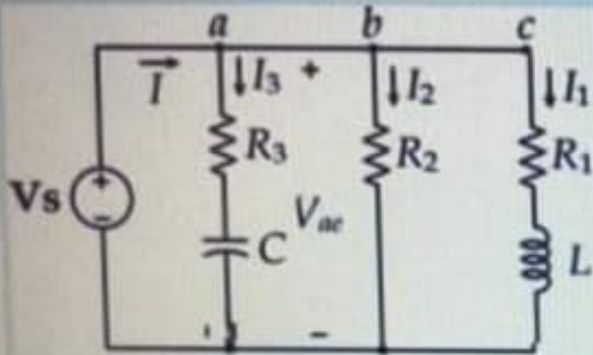According to the figure shown below, which statement is true:
(2 Points)



Assume V_s is DC
power supply

$$\cancel{R_3 = 2R_1 = 4R_2} \rightarrow \boxed{R_1 = 2R_2}$$

$$I_3 = 0 \rightarrow \text{open circuit}$$

$$I_1 = \frac{V}{2R_2} \quad I_2 = \frac{V}{R_2}$$

$$I_1 = \frac{1}{2} I_2$$

$$I_1 \text{ is half } I_2$$

☒ Both A and C are correct

☐ C. $I_3 = 0$

☐ D. I_1 is one fourth of I_2

☐ A. The current I_1 is half I_2

☐ B. The current I_1 is double of I_2


☐ Both B and C are correct

For a series R-L circuit :

(Note that you can select more than one choice if needed, but the wrong choice will cancel the correct one.)

(2 Points)

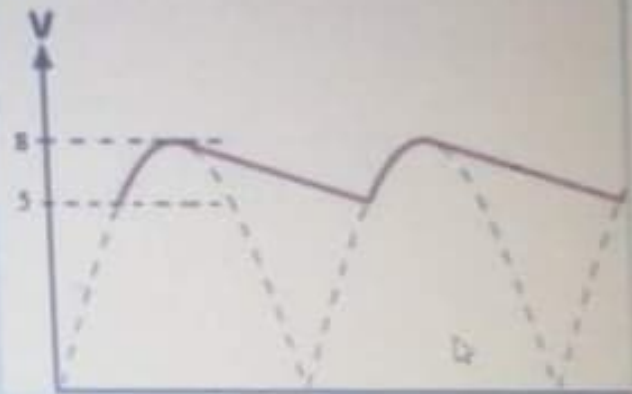- ☐ the power factor is equal one
- ☐ the total impedance Z is totally real
- ☐ None of the above
- ☒ the inductor impedance is maximum at high frequency
- ☒ the source current is maximum at low frequency



X

The output signal of a full-wave rectifier circuit with a filter is shown in the following figure.

The peak to peak ripple voltage (in volt) is:

(2 Points)

Enter your answer

18

As frequency decreases, which of the following statements is true? 
(2 Points)

- ☐ series RC impedance increases and parallel RC impedance decreases
- ☐ series RC impedance decreases and parallel RC impedance increases
- ☐ both series and parallel RC impedance increase
- ☐ None of these
- ☐ both series and parallel RC impedance decrease



For the circuit shown, if we want to find the phase shift between the source current and source voltage using the oscilloscope device, then we had to:


(2 Points)

V_s


I_s

∴ I_{source}

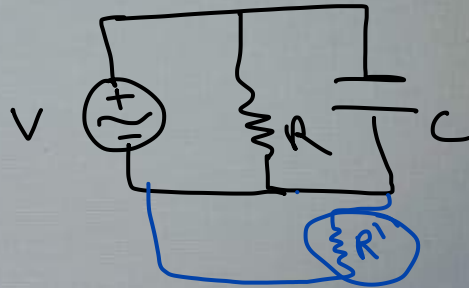- ☐ connect CH1 across V, and connect CH2 across C
- ☐ connect CH1 across V, and connect CH2 across R
- ☐ None of these
- ☒ An element to the circuit must be added and connect CH2 parallel to it while CH1 is connected to V
- ☐ connect CH1 across R, and connect CH2 in series with C
- ☐ connect CH1 across V, and connect CH2 in series with V



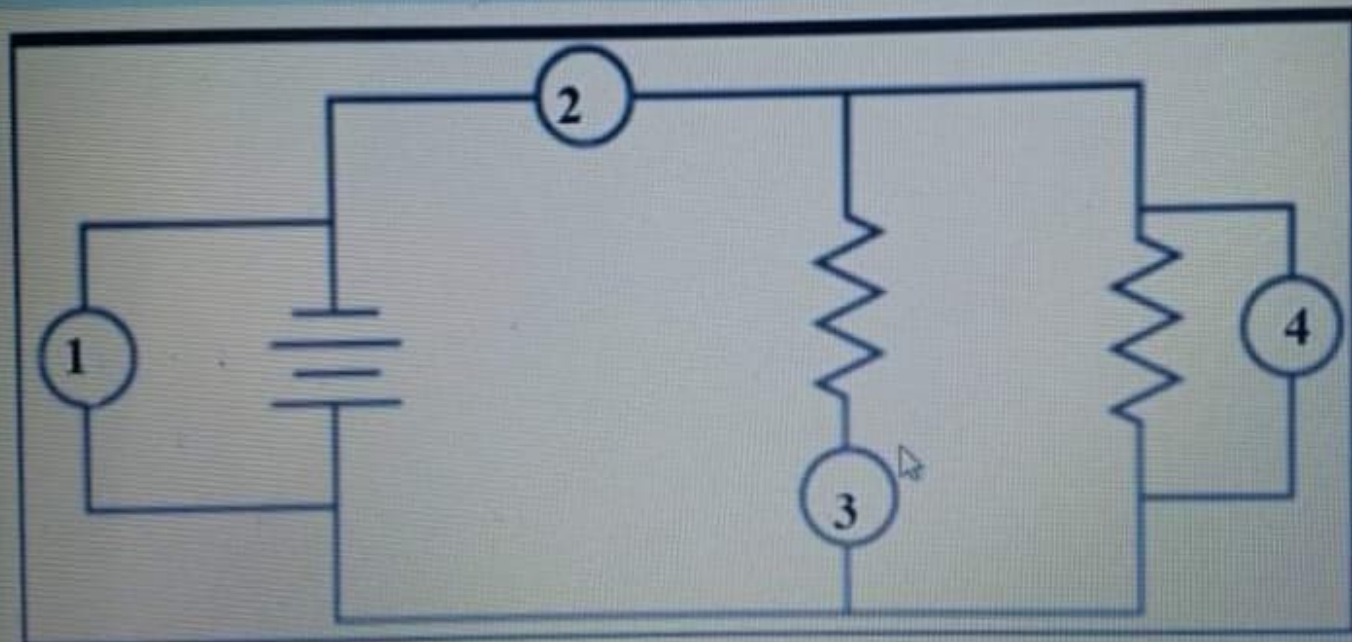You are asked to connect the following circuit in the lab, to connect it correctly: ☐
(1 Point)



☐ B. Devices 2 and 3 are ammeters. Devices 1 and 4 are voltmeters.

☐ A. Devices 1 and 4 are ammeters. Devices 2 and 3 are voltmeters.

- ☒ B. Devices 2 and 3 are ammeters, Devices 1 and 4 are voltmeters
- ☐ A. Devices 1 and 4 are ammeters, Devices 2 and 3 are voltmeters
- ☐ C. Devices 2 and 4 are ammeters, Devices 1 and 3 are voltmeters
- ☐ Both A and C are correct
- ☐ None of these.


Ammeter $\rightarrow$ (Series)
Voltmeter $\rightarrow$ (Parallel)

For a parallel R-L circuit, the correct statement is: 
(2 Points)

- ☐ V_s ^{lead} lag I
- ☐ As source frequency decrease, R will decrease
- ☐ As source frequency increase, X_L ^{increase} decrease
- ☐ None of these
- ☐ As source frequency increase, the inductor current will decrease

مسئله X

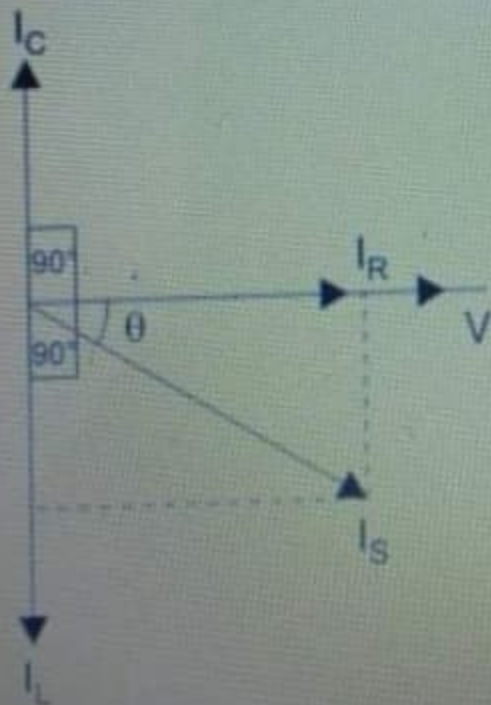For R-L-C parallel circuit, which is the correct statement:
(2 Points)



A. $I_s = (I_c - I_L) + I_R$


B. $I_s = (I_L - I_c) + I_R$

C. $I_s = (I_R - I_L) + I_c$

D. $I_s = (I_c - I_R) + I_L$

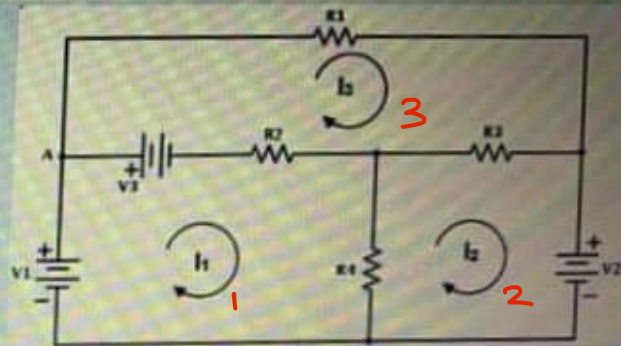E. A and B are correct

The correct mesh equation for mesh 2 is: 
(1.5 Points)



$$\underline{+V_2 + R_4(I_2 - I_1) + R_3(I_2 - I_3) = 0}$$

$$\underline{-V_2 = I_2(R_4 + R_3) - I_3(R_3) - R_4(I_1)}$$


☐ $V_1 - V_3 = I_1(R_2 + R_4) - (I_2)(R_4) - (I_3)(R_2)$

☒ $-V_2 = I_2(R_3 + R_4) - (I_3)(R_3) - (I_1)(R_4)$

☐ $V_2 = I_2(R_3 + R_4) - (I_3)(R_3) - (I_1)(R_4)$

☐ $V_3 = I_3(R_2 + R_3 + R_1) - (I_1)(R_2) - (I_2)(R_3)$

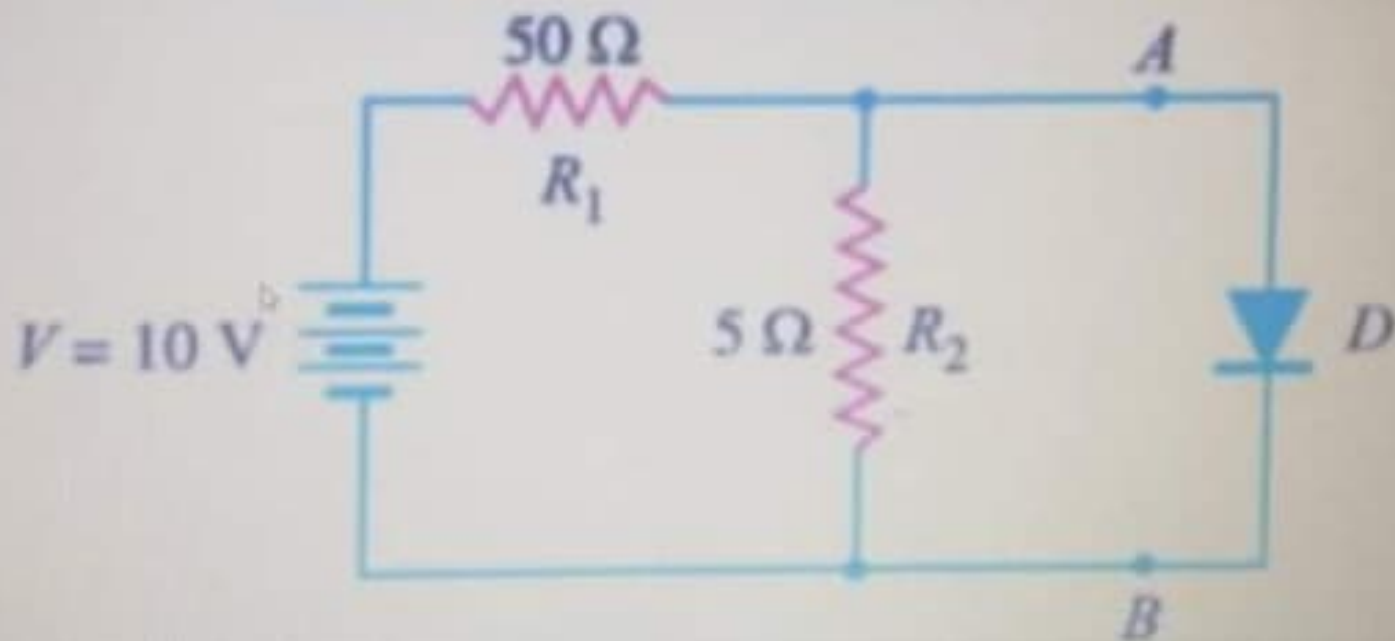18 Use the figure to answer the following questions, assume practical germanium diode ($V_f = 0.3 \text{ V}$)



19

The voltage (in volt) across 5 ohm resistor is
(2 Points)

~~Star~~ ??

☐ 0.3

☐ None of above