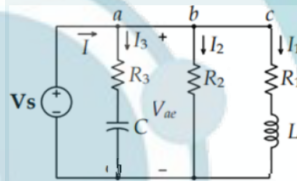


3

According to the figure shown below, which statement is true: ☐

(2 Points)



Assume V_s is DC power supply


$$R_3 = 2R_1 = 4R_2$$

- ☒ Both A and C are correct
- ☐ Both B and C are correct
- ☐ B. The current I_1 is double of I_2
- ☐ D. I_1 is one fourth of I_2
- ☐ C. $I_3 = 0$
- ☐ A. The current I_1 is half I_2

4

You are asked to connect the following circuit in the lab, to connect it correctly: ☐


(1 Point)

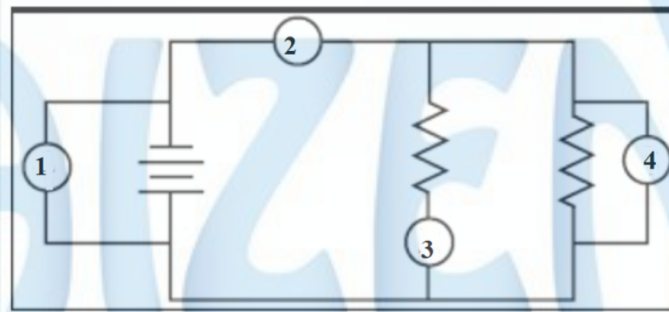

- ☐ A. Devices 1 and 4 are ammeters, Devices 2 and 3 are voltmeters
- ☐ B. Devices 2 and 3 are ammeters, Devices 1 and 4 are voltmeters
- ☐ Both A and C are correct
- ☐ C. Devices 2 and 4 are ammeters, Devices 1 and 3 are voltmeters
- ☐ None of these.

5

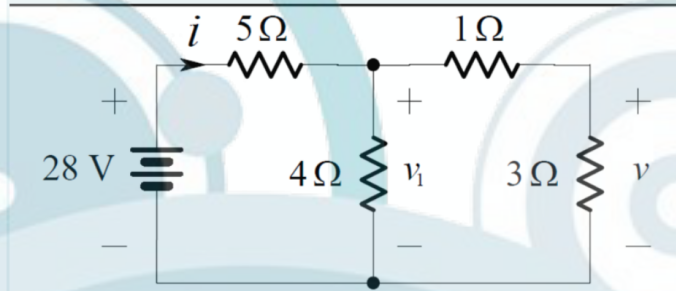According to the figure, which statement is correct: ☐ (1 Point)



- ☐ None of these
- ☐ C. The current through 4 ohm is equal to the current through 3 ohm
- ☐ A. The voltage across 4 ohm is higher than the voltage across 5 ohm
- ☐ B. The current through 4 ohm is higher than the current through 3 ohm
- ☐ Both A and C


6

For the shown function generator device, if you want to generate a square wave with 3000 Hz, which buttons you have to press: (1 Point)



- ☐ B then 4, then rotate the frequency knob
- ☐ None of the above
- ☐ A then 5, then rotate the frequency knob
- ☐ C then 4, then rotate the frequency knob
- ☐ A then 2, then rotate the frequency knob
- ☐ C then 2, then rotate the frequency knob

7

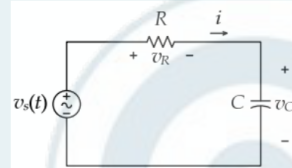


For the series RC circuit shown, given that the source frequency is 150 Hz, $R = 2000 \text{ ohm}$ and the total impedance phase angle is (-75°) degree. The capacitor C value is: (2 Points)

- ☐ 142.2 nF
- ☐ 1.422 nF
- ☐ 14.22 nF
- ☐ 142.2 microF
- ☐ None of the above

- ☐ None of the above

8

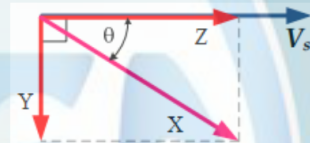

According to the phasor diagram for a parallel RL circuit shown, the symbols X, Y and Z are referred to: (2 Points)

- ☐ X is for inductor current, Y is for source current and Z is for the resistor current
- ☐ X is for resistor current, Y is for source current and Z is for the inductor current
- ☐ X is for source current, Y is for resistor current and Z is for the inductor current
- ☐ X is for source current, Y is for inductor current and Z is for the resistor current
- ☐ None of the above
- ☐ X is for resistor current, Y is for inductor current and Z is for the source current
- ☐ X is for inductor current, Y is for resistor current and Z is for the source current

- ☐ X is for inductor current, Y is for source current and Z is for the resistor current
- ☐ X is for resistor current, Y is for source current and Z is for the inductor current
- ☒ X is for source current, Y is for resistor current and Z is for the inductor current
- ☐ X is for source current, Y is for inductor current and Z is for the resistor current
- ☐ None of the above
- ☐ X is for resistor current, Y is for inductor current and Z is for the source current
- ☐ X is for inductor current, Y is for resistor current and Z is for the source current

9

The resistor voltage in a series RL circuit is always out of phase with the source current. ☐ (2 Points)

- ☐ True
- ☐ False

- ☐ L
- ☐ B

11


For a series R-L circuit :

(Note that you can select more than one choice if needed, but the wrong choice will cancel the correct one.) (2 Points)

- ☐ the inductor impedance is minimum at high frequency
- ☐ None of the above
- ☐ the total impedance Z is totally real
- ☐ the source current is maximum at low frequency
- ☐ the power factor is equal one



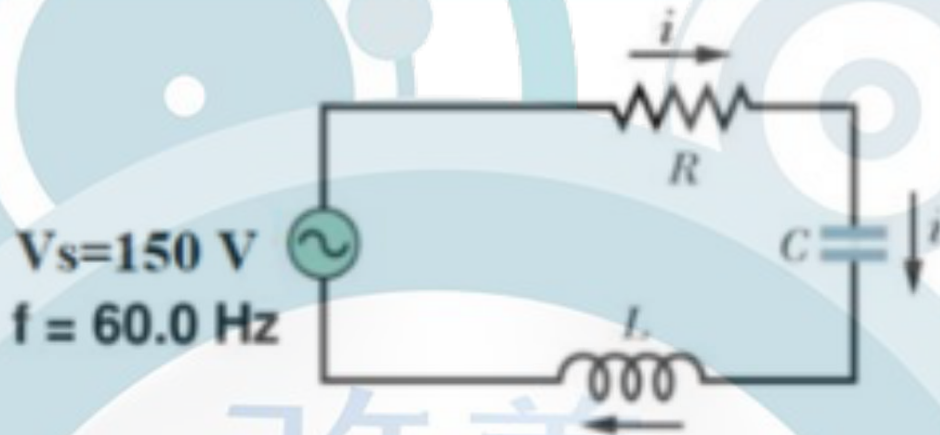
For the series R-L-C circuit shown, Given that $R=200\text{ ohm}$, $L = 1.5\text{ H}$ and $C = 3.5\text{ microfarad}$. answer the following questions:




12

The magnitude of total impedance in (ohm) is:
(2 Points)


- ☐ 54.68
- ☐ 303.62
- ☐ None of above
- ☐ 1529.92
- ☐ 1229

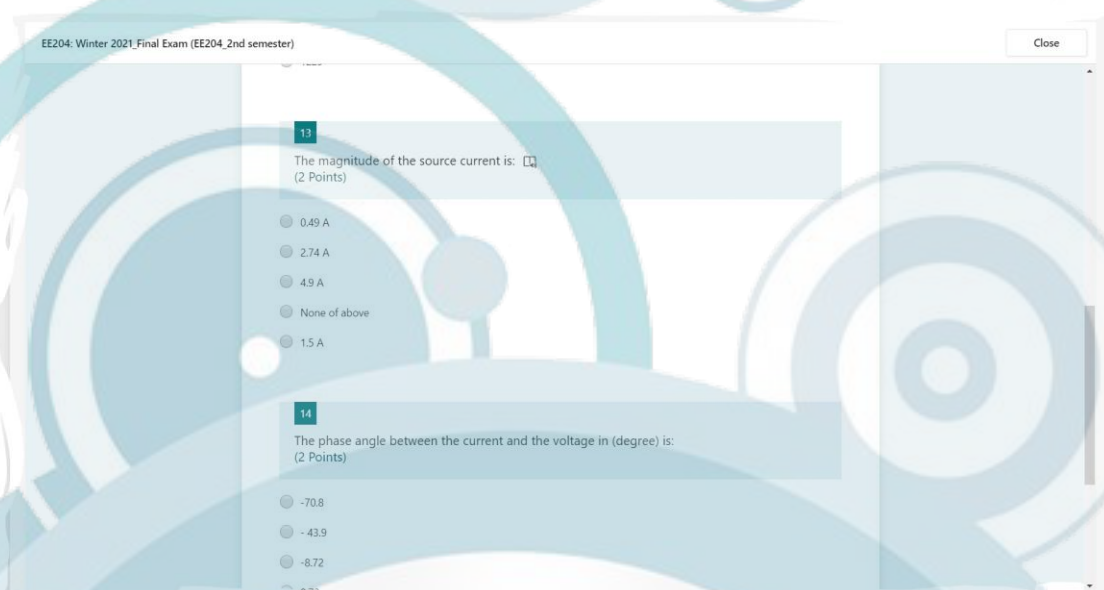

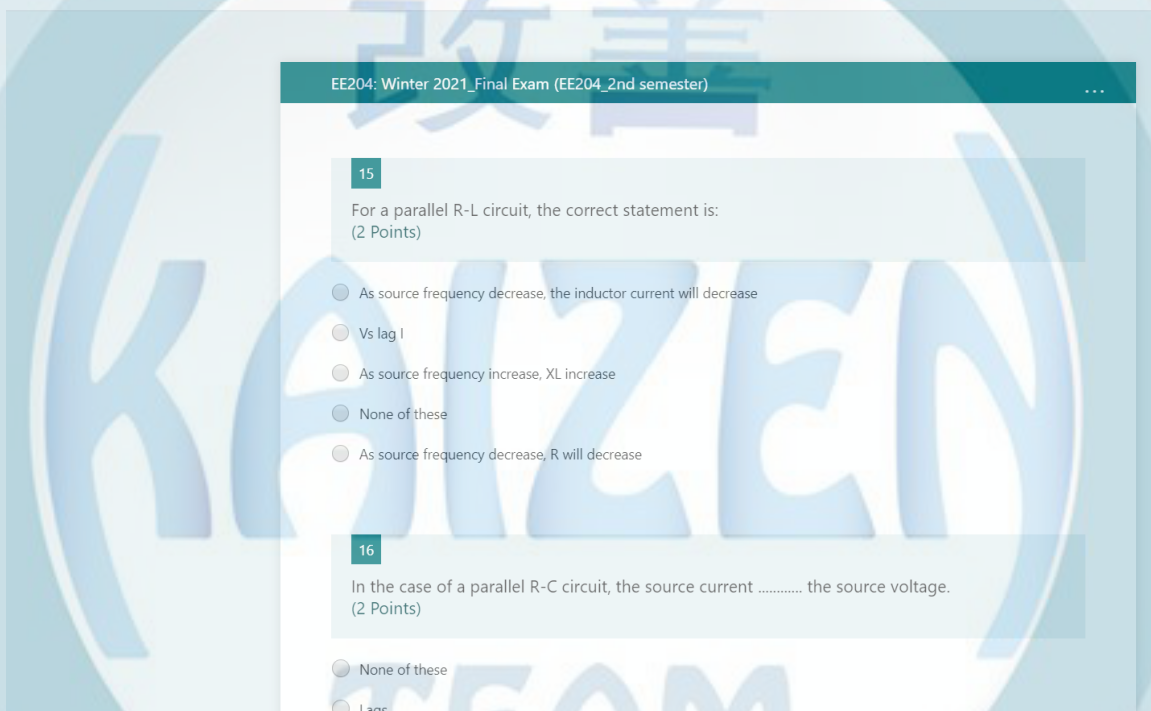EE204: Winter 2021 Final Exam (EE204_2nd semester)



17

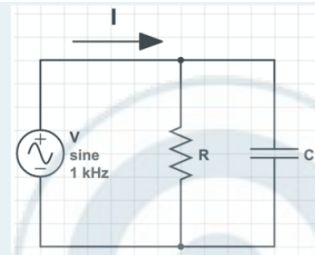

For the circuit shown, if we want to find the phase shift between the source current and the source voltage using the oscilloscope device, then we had to: ☐ (2 Points)

- ☒ connect CH1 across V, and connect CH2 in series with V
- ☐ connect CH1 across R, and connect CH2 in series with C
- ☐ An element to the circuit must be added and connect CH2 parallel to it while CH1 is connected to V
- ☐ connect CH1 across V, and connect CH2 across C
- ☐ None of these
- ☐ connect CH1 across V, and connect CH2 across R


18

As frequency decreases, which of the following statements is true? ☐ (2 Points)

- ☐ both series and parallel RC impedance decrease
- ☐ series RC impedance increases and parallel RC impedance decreases
- ☐ None of these
- ☐ series RC impedance decreases and parallel RC impedance increases
- ☐ both series and parallel RC impedance increase



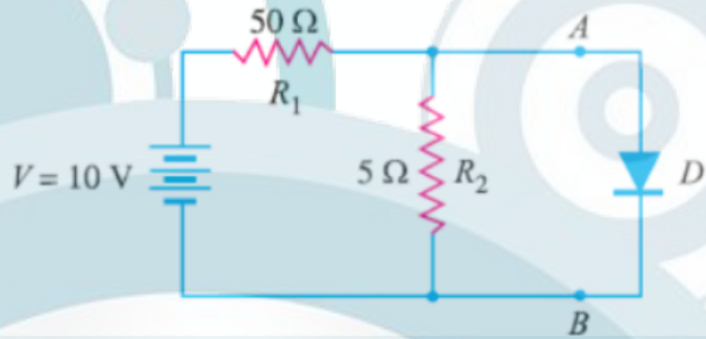Use the figure to answer the following questions, assume practical germanium diode ($V_y = 0.3 \text{ V}$)



19


The voltage (in volt) across 5 ohm resistor is:

(2 Points)

- ☐ None of above
- ☐ 0.3
- ☐ 0.809
- ☐ 0.909
- ☐ 0.7
- ☐ 0.55



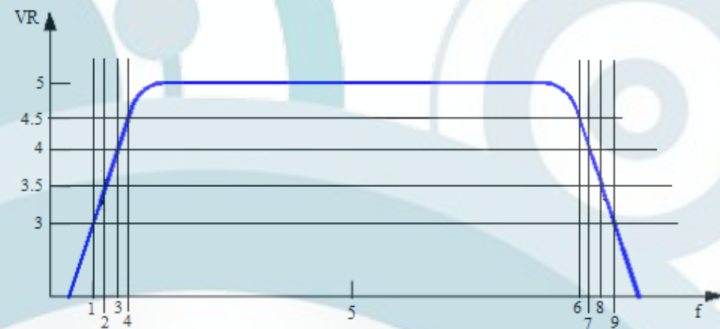For a series R-L-C circuit, the resistor voltage variation with frequency is shown in the figure, answer the following questions:



23

The lower and upper cutoff (corner) frequencies, respectively (f_L and f_H) are: (2 Points)

- ☐ None of the above
- ☐ 4 and 6
- ☒ 2 and 8
- ☐ 1 and 9
- ☐ 3 and 7
- ☐ 5 only

24

The voltage at the resonance frequency is: (1 Point)

- ☐ 3
- ☐ 4.5
- ☐ 5
- ☒ 3.5