three sensors are attached to a printing device, with three alarms attached to the sensors. The first sensor 'h' detects if the device needs ink. The second sensor 'B' detects if the device needs repair. The third sensor 'C' detects if the device should jam. An alarm sounds if 2 or more problems occur

```
when B=1 \Rightarrow the device needs inK, otherwise B=0 when C=1 \Rightarrow the device needs repair, otherwise B=0 when C=1 \Rightarrow the device should jam, otherwise C=0
```

alarm X = I when two or more problems occur

$$X = AB\overline{C} + A\overline{B}C + \overline{A}BC + ABC$$

$$= AB (\overline{C} + C) + A\overline{B}C + \overline{A}BC$$

$$= AB + ABC + \overline{A}BC$$

$$= A(B + \overline{B}C) + \overline{A}BC$$


$$= A(B + \overline{B}C) + \overline{A}BC$$

$$= AB + AC + \overline{A}BC$$

$$= AB + C(A + \overline{A}B)$$

$$= AB + C(A + \overline{A}C) + ABC$$

$$= AB + C(A + \overline{A}C) + ABC$$

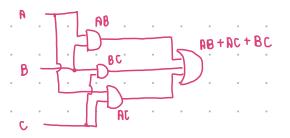

Schools are given snow days given specific circumstances. If there is ice on the roads, but no salt, then a snow day is given. If there is salt however, then a snow day is not given. Regardless of whether or not there is salt, whenever there is >2 inches of snow, then a snow day is given.

A computer chip controls whether or not children are allowed to watch a specific TV show. If the time is before 5PM, then the TV always works. However, if it's after 5PM, then the shows rating is used. If the rating is for General Audiences, then the TV will work; however, if the rating is for Mature Audiences, then the TV does not turn on

```
B=1 \Rightarrow \text{ before 5PM } \Rightarrow \text{ else } B=0
G=1 \Rightarrow \text{ rating for general audiences} \Rightarrow \text{ else } G=0
M=1 \Rightarrow \text{ rating for mature audiences} \Rightarrow \text{ else } M=0
```

$$X = BG\overline{M} + \overline{B}G\overline{N} + BG\overline{N} + BG\overline{N} + BG\overline{M} + BG\overline{M}$$

$$= BG\overline{(N+M)} + BG\overline{(M+M)} + \overline{B}G\overline{M}$$


$$= BG\overline{+} BG + \overline{B}G\overline{M}$$

$$= BG\overline{+} BG\overline{M}$$

$$= BG\overline{+} BG\overline{+} BG\overline{M}$$

$$= BG\overline{+} BG\overline{+} BG\overline{+} BG\overline{+} BG\overline{M}$$

$$= BG\overline{+} BG\overline{+}$$

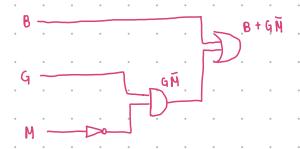

B + G N