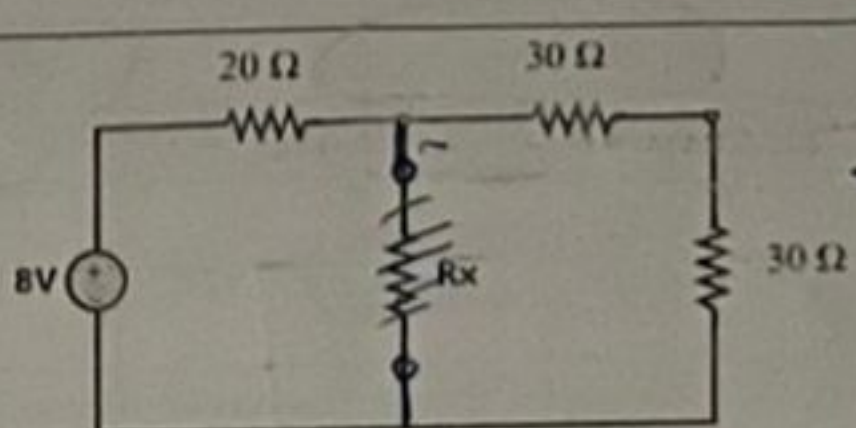
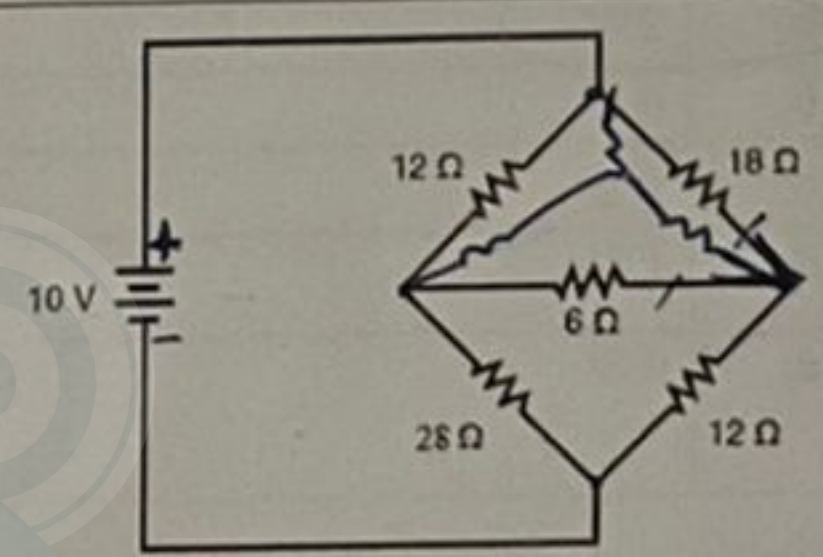
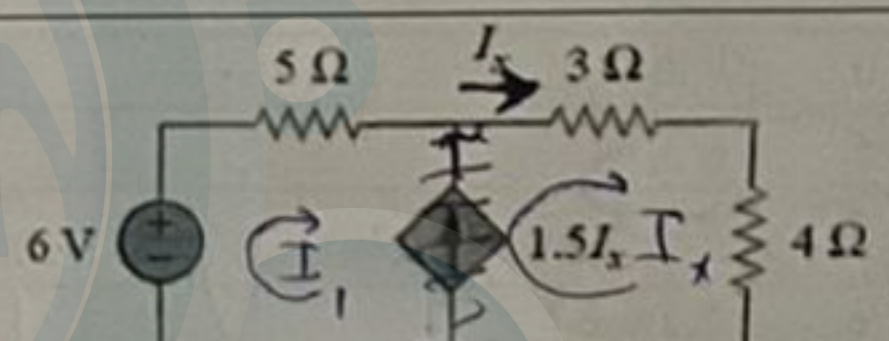



Q7	If you replace $R_x$ in the following circuit by an open circuit, the driven current by the source is:	
a.	0.1 A	 $\frac{8}{80} =$
b.	0.133 A	
c.	0.4 A	
d.	8 A	
e.	0 A	

Q8	Use $\Delta$ -Y transformation to find the equivalent resistance seen by the 10V source for the circuit shown.	
a.	8 $\Omega$	
b.	76 $\Omega$	
c.	14.62 $\Omega$	
d.	16 $\Omega$	
e.	21.6 $\Omega$	


Q9	For the circuit shown, the current $I_x$ is:	
a.	0.857 A	 $I_x = 1.5I_x \cdot \frac{5}{12}$
b.	1.33 A	
c.	0.5 A	
d.	1 A	
e.	0 A	

Handwritten solution for Q8:

Initial circuit diagram for Q8:

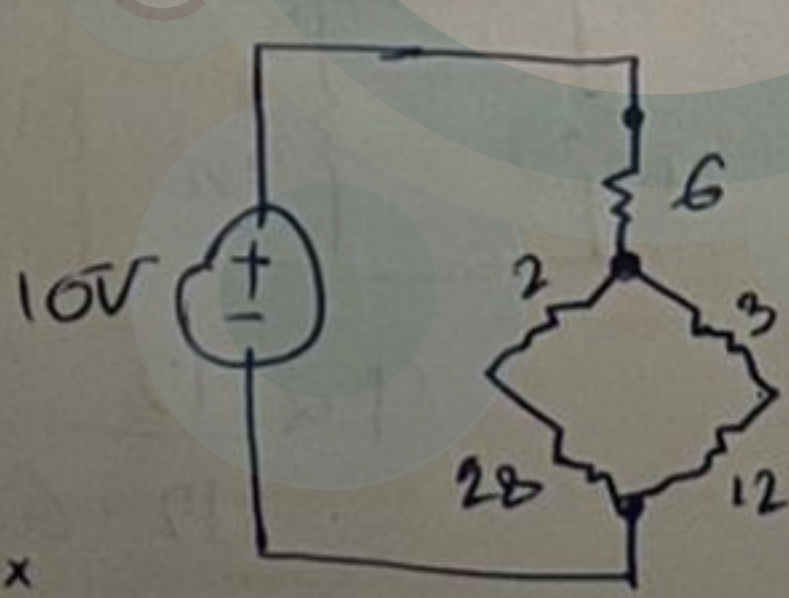

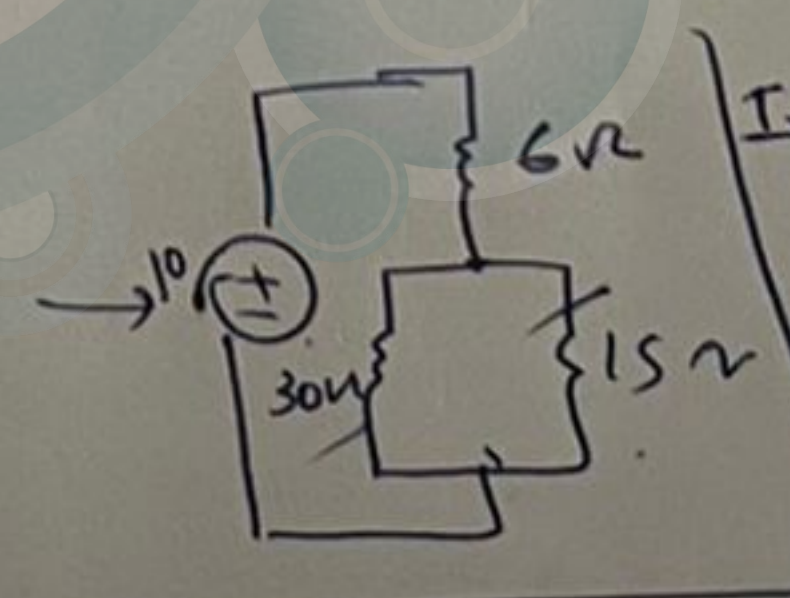Equivalent circuit diagram after  $\Delta$ -Y transformation:



Handwritten equations:

$$I_x = 1.5I_x \cdot \frac{5}{12}$$

$$(1.5 - 1)I_x = \frac{5}{12}$$

$$0.5I_x = \frac{5}{12}$$

$$I_x = \frac{5}{6} = 0.833 \text{ A}$$

Handwritten equations for Q9:

$$1.5I_x = I_x + I_1 \quad \text{--- (1)}$$


$$-6 + 5I_1 + 3I_x + 5I_x = 0 \quad \text{--- (2)}$$

$$(1.5 - 1)I_x + I_1 = 0 \quad \text{--- (3)}$$


$$8I_x + 5I_1 = 6$$




10

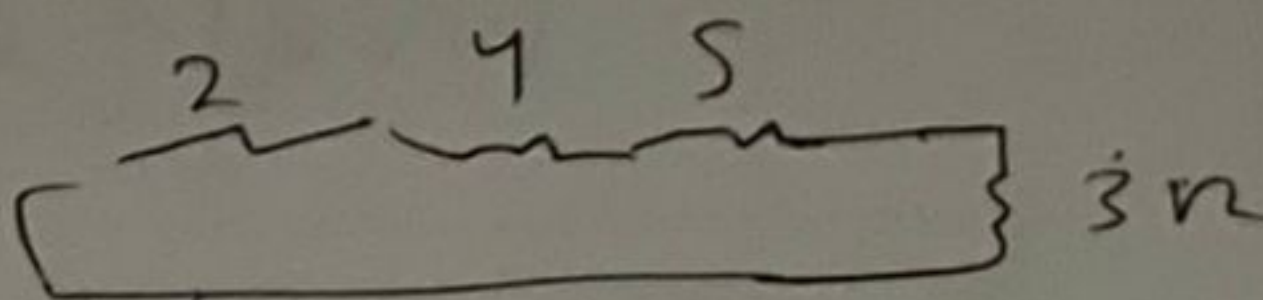


Q1	For the circuit shown, the voltage $v_x$ is:	
a.	2 V	
b.	2.86 V	
c.	2.5 V	
d.	1 V	
e.	0 V	

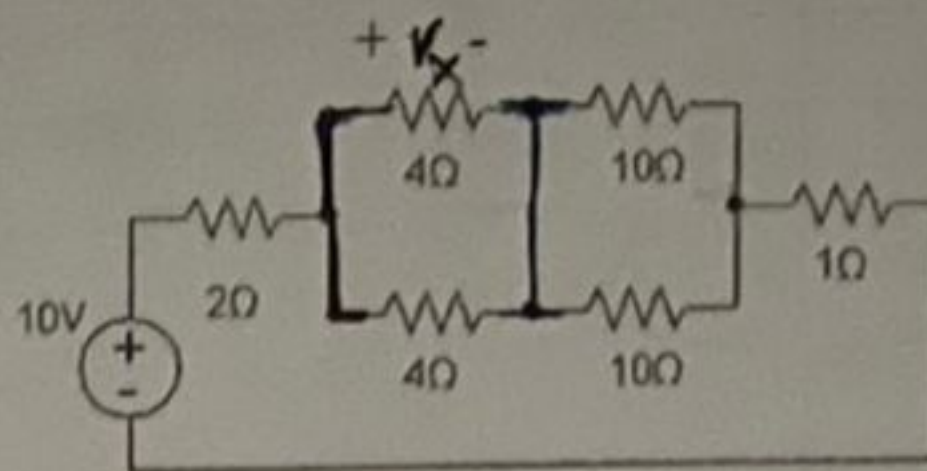

Q2	For the circuit shown, $I_o$ is:	
a.	0.5 A	
b.	1.5 A	
c.	0.33 A	
d.	1 A	
e.	0 A	

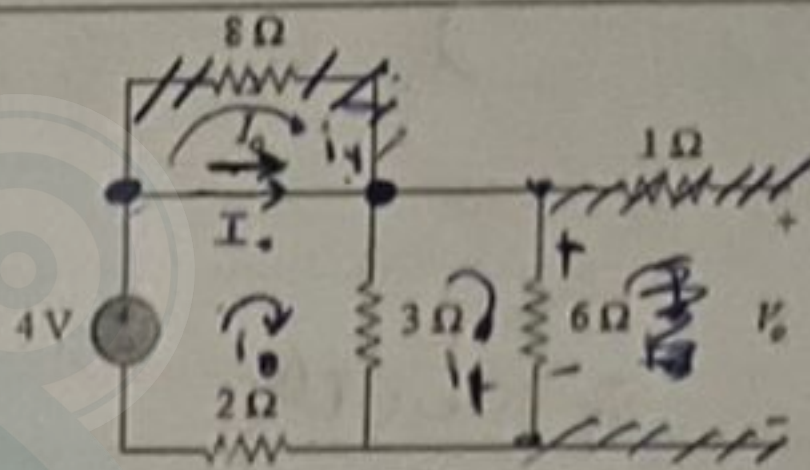


Q3	If you replace $R_x$ in the following circuit by a <u>short circuit</u> , the driven current by the source is:	
a.	0.133 A	
b.	0 A	
c.	0.4 A	
d.	0.1 A	
e.	None of these	

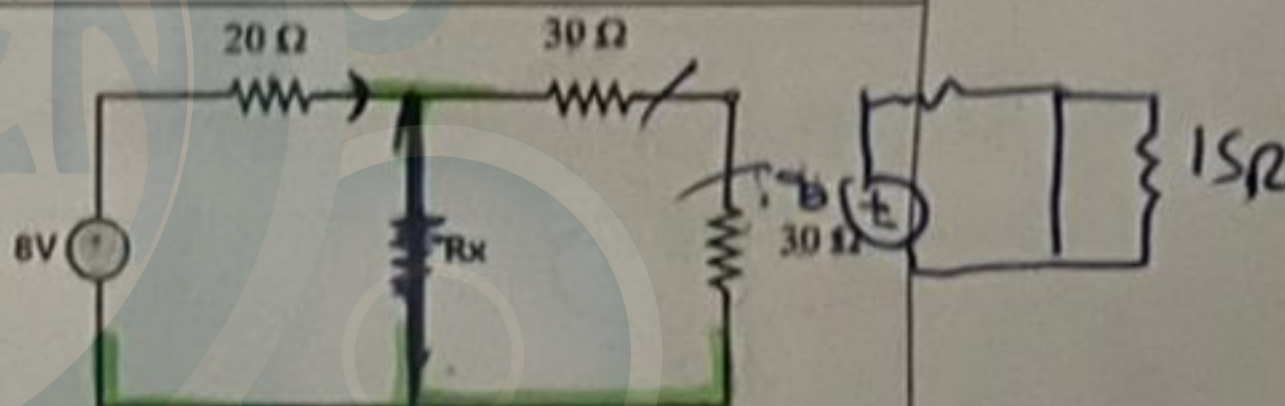

$$-4 + 3(I_1 - I_2) + 2I_1 = 0$$

$$I_1 = I_2$$

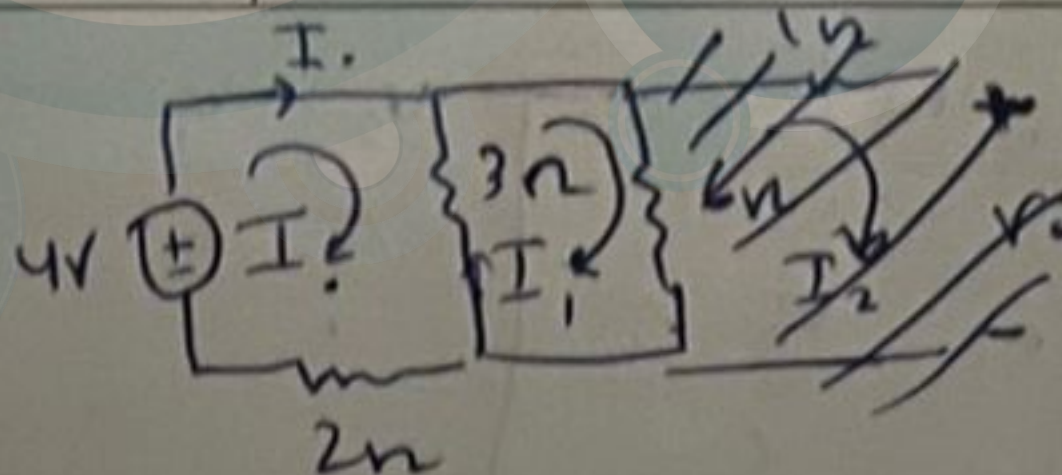

$$-4 + 3(I_1 - I_2) + 2I_1 = 0 \quad \text{--- (1)}$$


$$5I_1 - 3I_2 = 4 \quad \text{--- (1)}$$

$$I_1 = 1 \text{ A}$$

$$I_2 = 1/3 \text{ A}$$

$$6(I_1 - I_2) + 3(I_1 - I_2) = 0 \quad \text{--- (2)}$$

$$I_2 = 1/3 \text{ A}$$

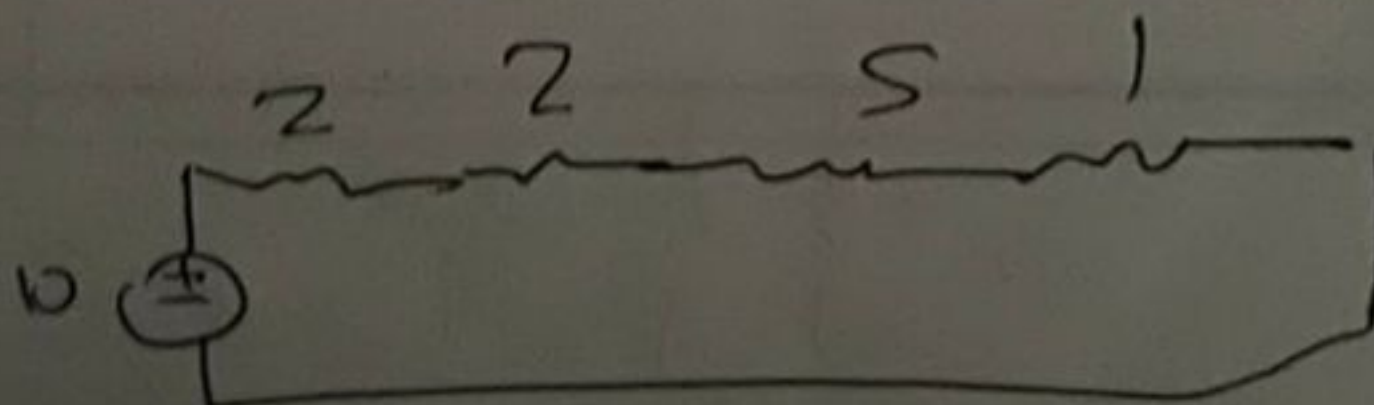




10V (1/6)

Q4 For the circuit shown, the voltage across the 6Ω resistor is:

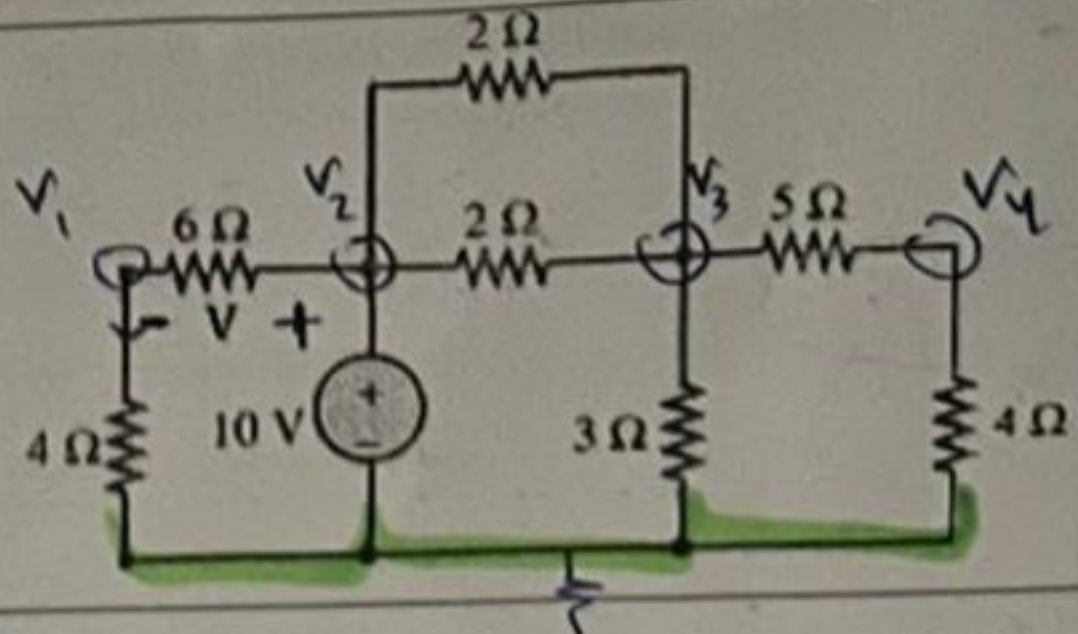
- a. 4 V
- b. 10 V
- c. -10 V
- d. -6 V
- e. 6 V



Q5 If the voltage across a resistor is 0.6V, and  $R=20\text{ K}\Omega$ , the current flowing through the resistor is

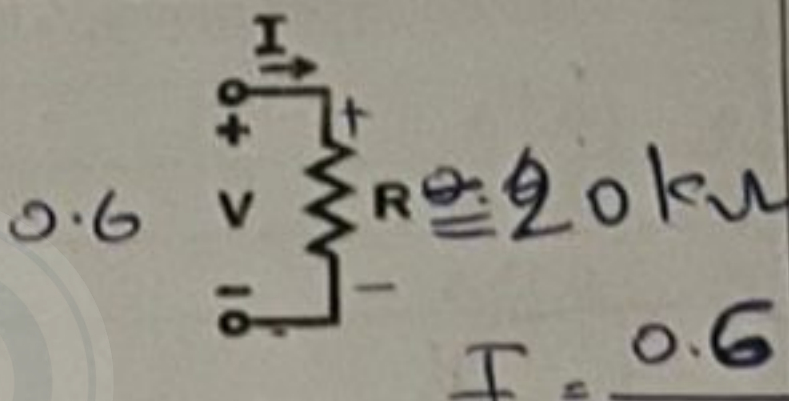
- a. 30 pA
- b. 30 μA
- c. 0.3 pA
- d. 0.3 μA
- e. 30 mA

$0.03 \times 10^{-3}$   
 $0.3 \times 10^{-4}$









Q6 For the circuit shown, the absorbed power in the 3k ohm resistor

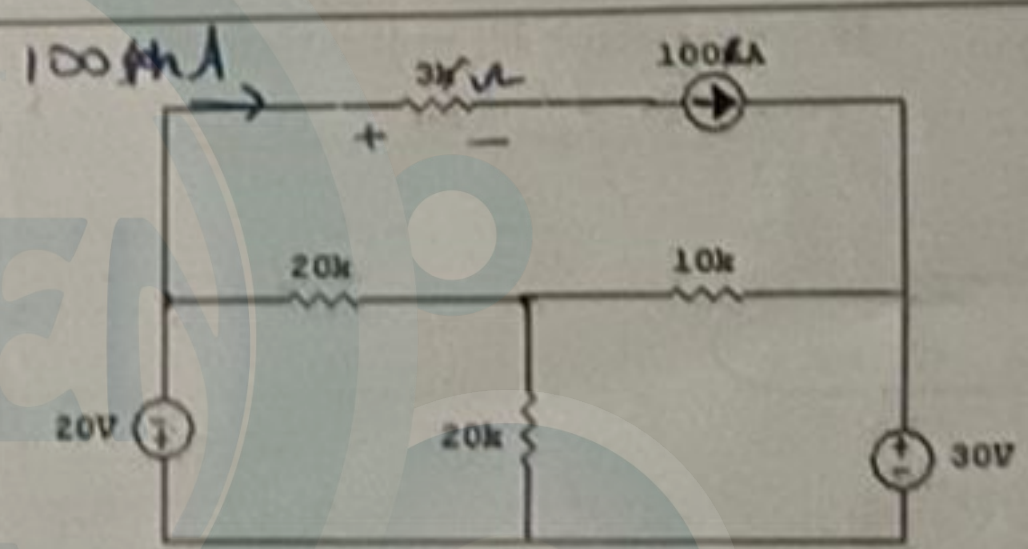- a. 900 W
- b. 3.333 μW
- c. 33.3 mW
- d. 300 W
- e. 30 W



$V_2 = +10V$

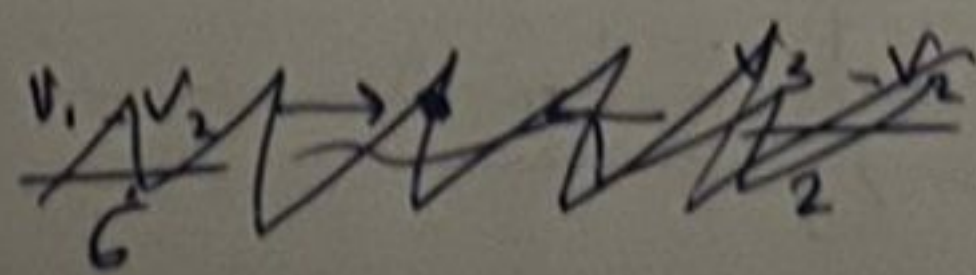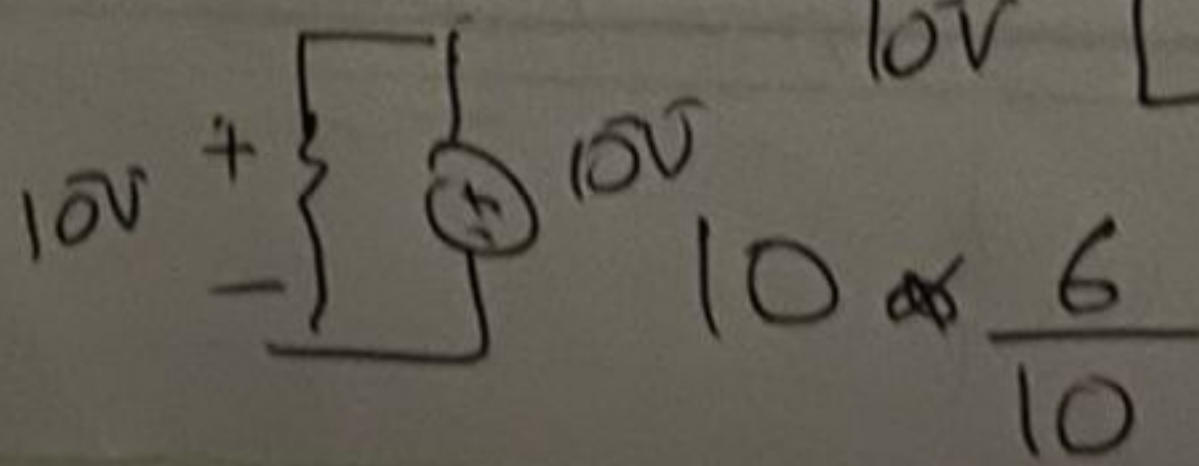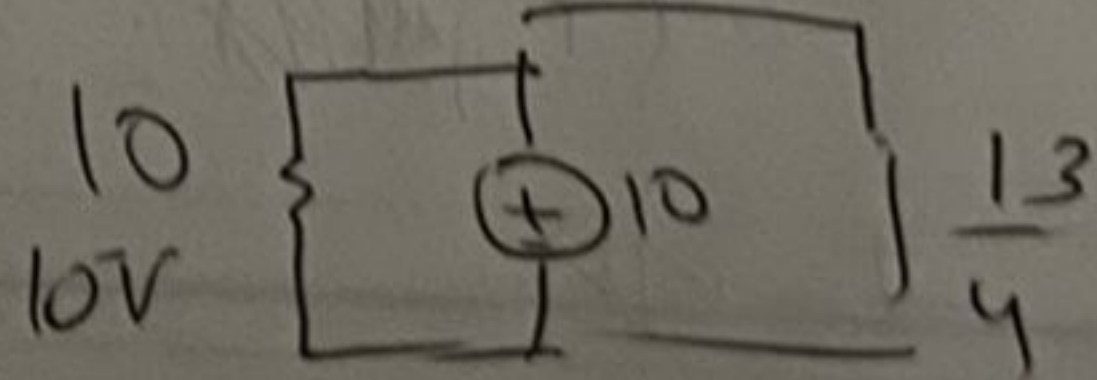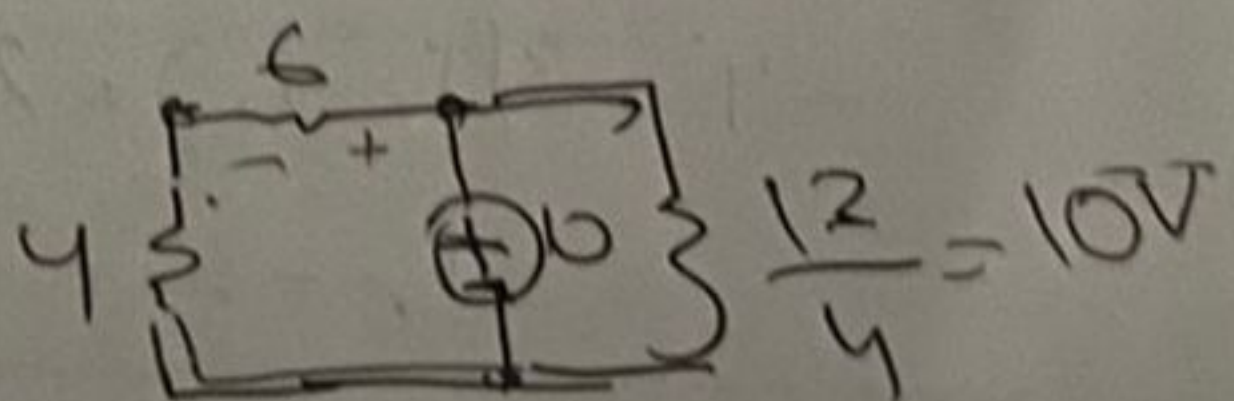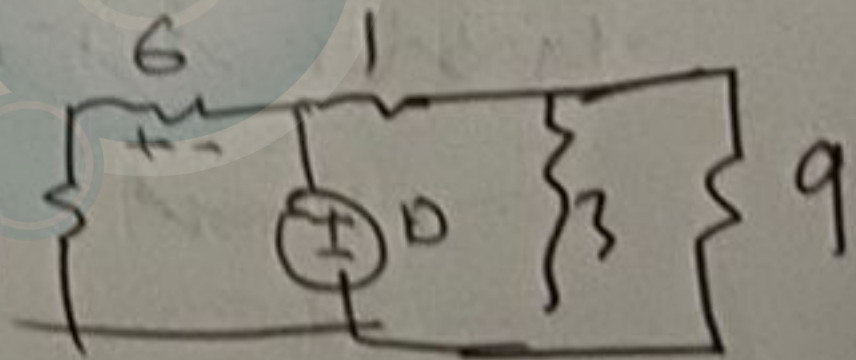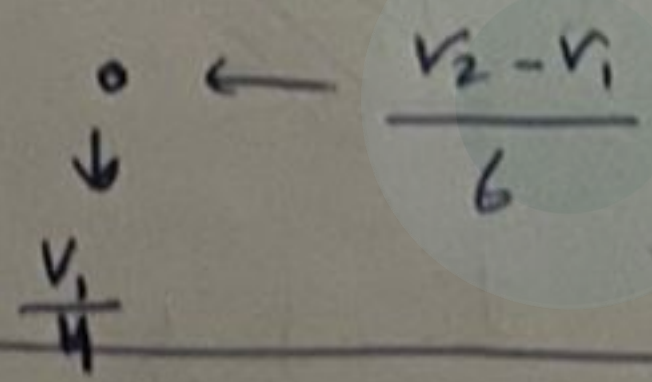$\frac{V_2 - V_1}{6} - \frac{V_1}{4} = 0$







$$I_x = \frac{V_1}{5} = \frac{-25}{5}$$

\*\* For the circuit shown, use Nodal Analysis to answer questions (13-16)

$$V_2 - V_1 = 0.2 \times \frac{V_1}{5}$$

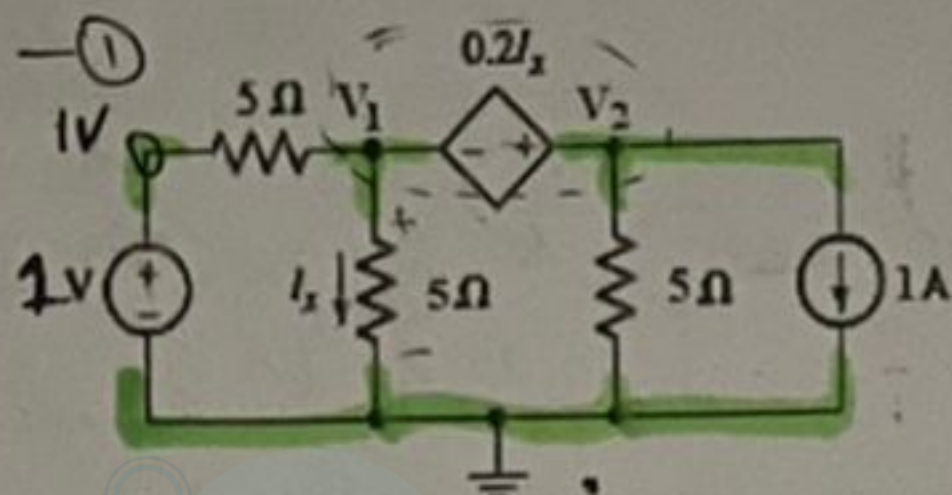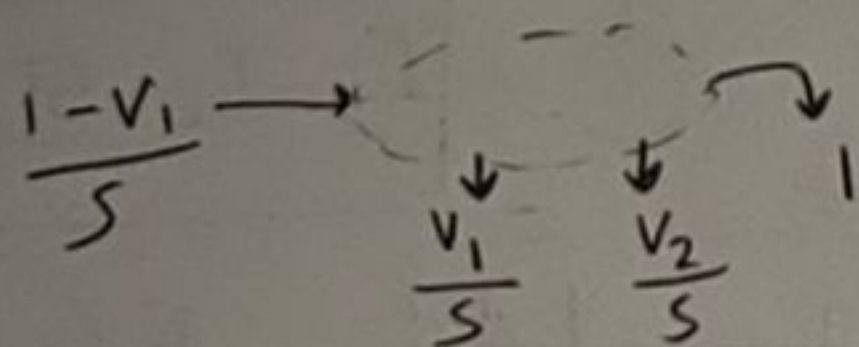

$$\frac{1-V_1}{5} - 1 - \frac{V_1}{5} - \frac{V_2}{5} = 0$$

$$\left(-\frac{1}{5} - \frac{1}{5}\right)V_1 - \frac{V_2}{5} = 1 - \frac{1}{5}$$

$$\left(-1 - \frac{0.2}{5}\right)V_1 + V_2 = 0$$

Q13	The nodal voltage $V_1$ is:
a.	-2.632 V
b.	2.632 V
c.	-1.316 V
d.	1 V
e.	0.2 V

Q14	The current $I_x$ is:
a.	3.375 A
b.	-0.2632 A
c.	-3.375 A
d.	1.37 A
e.	-0.844 A

Q15	The voltage at the reference point is:
a.	1 V
b.	-1 V
c.	5 V
d.	-5 V
e.	0 V

Q16	The nodal voltage $V_2$ is:
a.	6.75 V
b.	1 V
c.	-1.37 V
d.	-4.22 V
e.	0.3 V




$$-6 + 5I_1 + 3I_x + 4I_x = 0 \rightarrow I_x = 1.33$$

$$1.5I_x = I_x - I_1 \rightarrow I_1 = -2/3$$

Q10	For the circuit shown, the absorbed or generated power of the 6V source is:	
a.	4 W, absorbed	
b.	4 W, generated	
c.	8 W, generated	
d.	8 W, absorbed	
e.	None of these	

Q11	For the circuit shown, $V_o$ is:	
a.	2 V	
b.	4 V	
c.	3 V	
d.	1 V	
e.	0 V	

Q12	For the circuit shown, the current through the 6-Ω resistor $I$ is:	
a.	3 A	
b.	9 A	
c.	6 A	
d.	1.5 A	
e.	5.14 A	

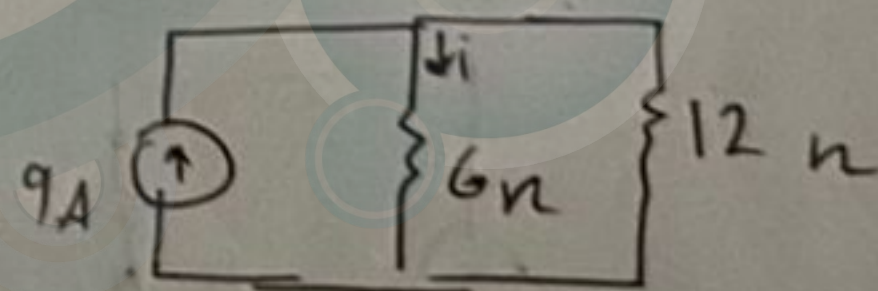

$$9 \times \frac{12}{12+6}$$