

Q9	Thevenin equivalent voltage is:	
a.	24 V	
b.	-24 V	
c.	36 V	
d.	12 V	
e.	-12 V	


Q10	Thevenin equivalent resistance to the left of R_L is:	
a.	0Ω	
b.	4Ω	
c.	2Ω	
d.	6Ω	
e.	1.33Ω	


$$i = C \frac{dv}{dt}$$


Q11	If $C=0.2F$ and $v(t) = e^{-2t}V$ in the following figure, then the current through the capacitor is:	
a.	$i(t) = 5e^{-2t} A$	
b.	$i(t) = -0.4e^{-2t} A$	
c.	$i(t) = -0.1e^{-2t} A$	
d.	$i(t) = e^{-2t} A$	
e.	$i(t) = 0.2e^{-2t} A$	

$$i = (0.2) \times e^{-2t} \times -2$$

$$i = C \left(\frac{dv}{dt} \right)$$

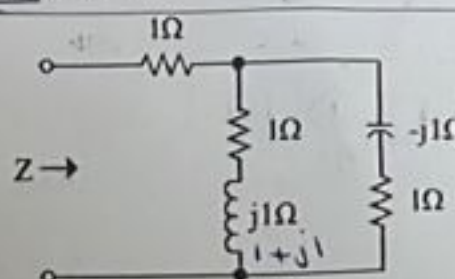Q19	For the circuit shown below, the equivalent impedance Z is ...	
a.	$1\ \Omega$	
b.	$2\ \Omega$	
c.	$3\ \Omega$	
d.	$3 + j2\ \Omega$	
e.	$1.5\ \Omega$	

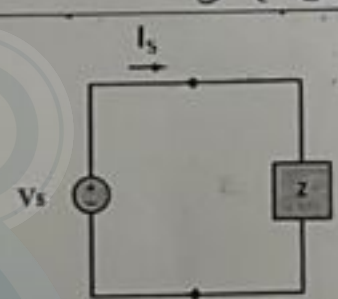Q20	For the circuit shown below, if $v_s(t) = 10 \cos(10t)$ and $i_s(t) = 5 \sin(10t + 30^\circ)$, the elements of the impedance Z are and	
a.	$R=1\ \Omega$ and $C=0.173\ \text{F}$	
b.	$R=2\ \Omega$ and $C=0.173\ \text{F}$	
c.	$R=1\ \Omega$ and $L=1.73\ \text{H}$	
d.	$R=1\ \Omega$ and $C=1.73\ \text{F}$	
e.	$R=1\ \Omega$ and $L=0.173\ \text{H}$	

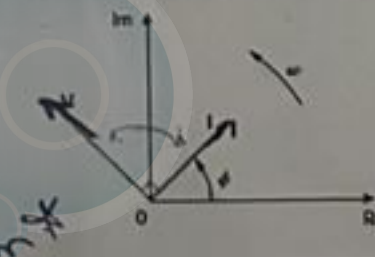Q21	The phasor diagram shown below shows the phasor relation between the voltage and current phasors \mathbf{V} and \mathbf{I} of ac circuit element. This element is	
a.	combined (RL)	
b.	combined (RC)	
c.	pure inductor (L)	
d.	pure capacitor (C)	
e.	pure resistor (R)	

the answer

$\theta = 90^\circ$
 pure inductor
 $V \angle 0^\circ$
 $I \angle 90^\circ$
 $V \angle 0^\circ$
 $I \angle 90^\circ$

$$v_1(t) = 20 \cos(\omega t - 30^\circ) = 20 \angle -30^\circ$$

$$v_2(t) = 60 \cos(\omega t - 10^\circ) = 60 \angle -10^\circ$$



Q16	For the voltage waveforms $v_1(t) = 20\sin(\omega t + 60^\circ)$ V and $v_2(t) = 60\cos(\omega t - 10^\circ)$, the phase relation can be stated as		
a.	$v_1(t)$ leads $v_2(t)$ by 20°	b.	$v_1(t)$ leads $v_2(t)$ by 70°
c.	$v_1(t)$ lags $v_2(t)$ by 70°	d.	$v_1(t)$ lags $v_2(t)$ by 20°
e.	$v_1(t)$ lags $v_2(t)$ by 50°	f.	None of these

Q17	The sinusoidal waveform corresponding to a voltage phasor $V = 60\angle 15^\circ$ V, with angular frequency $\omega = 10$ rad/s is given by ... $60(10t + 15)$		
a.	$v(t) = 60\sin(10t + 15^\circ)$ V	<input checked="" type="radio"/> b.	$v(t) = 60\cos(10t + 15^\circ)$ V
c.	$v(t) = 60\sin(10t - 75^\circ)$ V	<input type="radio"/> d.	$v(t) = 60\cos(10t - 75^\circ)$ V
e.	$v(t) = 60\cos(10t - 75^\circ)$ V	f.	None of these

Q18	For the sinusoidal current waveform shown below, the waveform can be expressed as...	
a.	$i(t) = 20\sin(20\pi t - 45^\circ)$ A	<p>$\phi = +45^\circ$ $T = 100 \text{ ms}$</p>
b.	$i(t) = 20\sin(100t - 45^\circ)$ A	
c.	$i(t) = 20\cos(20\pi t + 45^\circ)$ A	
d.	$i(t) = 20\cos(100t - 45^\circ)$ A	
e.	$i(t) = 20\sin(20\pi t + 45^\circ)$ A	


20/10/11

$\omega = \frac{2\pi}{T} = \frac{2\pi}{100 \times 10^{-3}} = 20\pi \text{ rad/s}$
 $\phi = +45^\circ$
 $i(t) = 20\sin(20\pi t + 45^\circ)$ A

**For the circuit shown, answer questions (22-25)

$$Z\left(\frac{1}{12F}\right) = \frac{1}{\frac{1}{12}(4)} -j = -j3 \Omega$$

$$Z(3H) = 3(4)j = 12j \Omega$$

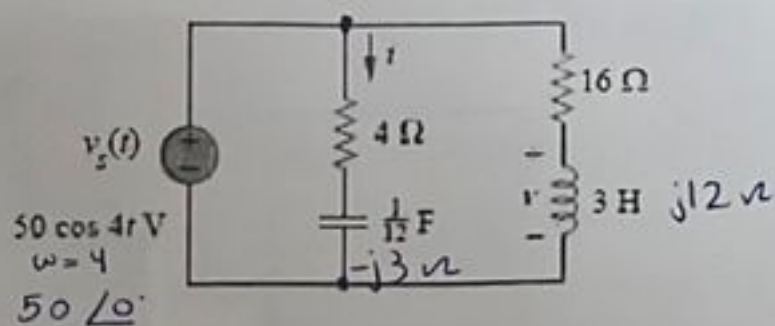


Q22	The impedance of the $\frac{1}{12}F$ is:			
a.	$-j3 \Omega$	b.	$j3 \Omega$	
c.	$-j\frac{1}{48}\Omega$	d.	$j\frac{1}{48}\Omega$	
e.	$-j1.333 \Omega$	f.	$j1.333 \Omega$	

Q23	The impedance of the $3H$ is:			
a.	$-j3 \Omega$	b.	$j3 \Omega$	
c.	$-j12 \Omega$	d.	$j12 \Omega$	
e.	$-j1.33 \Omega$	f.	$j1.33 \Omega$	



Q24	For the current waveforms $i(t)$ through the 4Ω resistor is:			
a.	$i(t) = 5\cos(4t) A$	b.	$i(t) = 10\cos(4t + 36.8^\circ) A$	
c.	$i(t) = 5\cos(4t - 90^\circ) A$	d.	$i(t) = 20\cos(4t + 45^\circ) A$	
e.	$i(t) = 10\cos(4t - 36.8^\circ) A$	f.	$i(t) = 10\cos(4t + 45^\circ) A$	

Q25	For the voltage waveforms across the inductor $v(t)$ is:			
a.	$v(t) = 6\cos(4t + 15^\circ) V$	b.	$v(t) = 30\cos(4t - 53.1^\circ) V$	
c.	$v(t) = 50\cos(4t + 90^\circ) V$	d.	$v(t) = 30\cos(4t + 53.1^\circ) V$	
e.	$v(t) = 50\cos(4t - 90^\circ) V$	f.	$v(t) = 6\cos(4t + 15^\circ) V$	

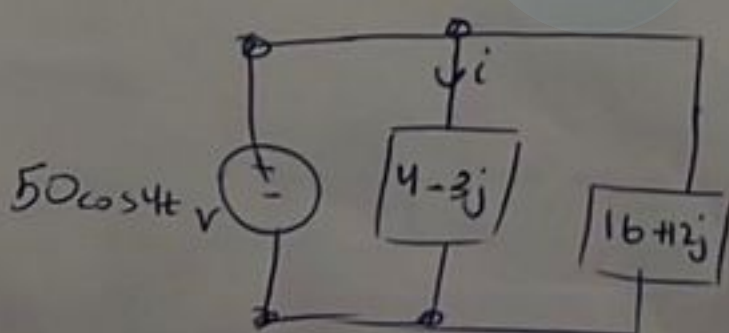

Best Wishes

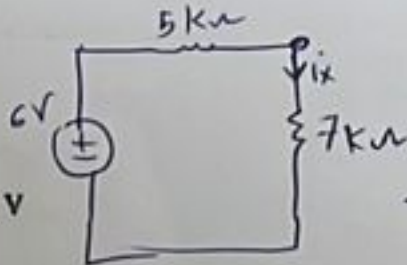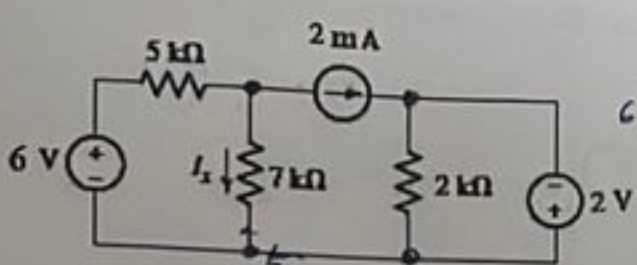**For the circuit shown, use Superposition principle to answer questions (12-15)





$$I_{x1} =$$


$$-6 \times 5 I_x + 7 I_x = 6$$

$$12 I_x = 6 \Rightarrow I_x = 0.5 \text{ mA}$$



Q12	The current I_x due to the <u>2V</u> voltage source:
a.	1 mA
b.	-1 mA
c.	-0.5 mA
d.	0 A
e.	0.5 mA

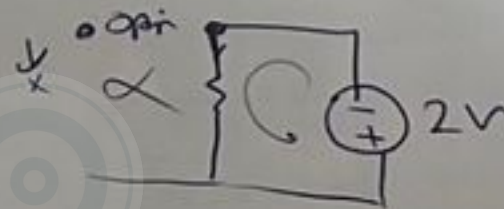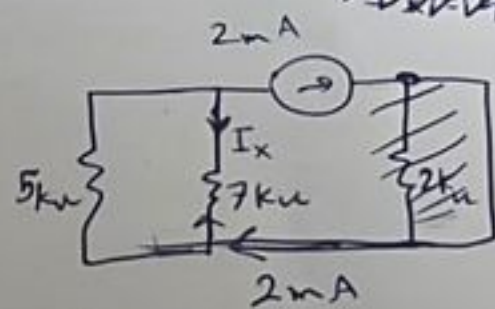

Q13	The current I_x due to the 6V voltage source:
a.	0.857 mA
b.	1.2 mA
c.	6 mA
d.	0 A
e.	0.5 mA

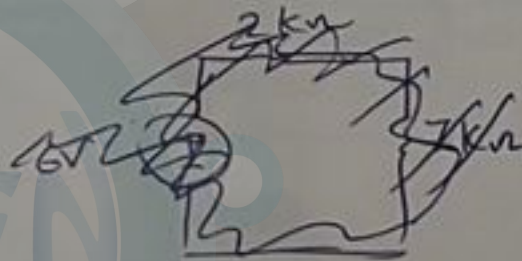

Q14	The current I_x due to the 2mA current source:
a.	-2 mA
b.	-0.286 mA
c.	0 A
d.	2 mA
e.	-0.83 mA

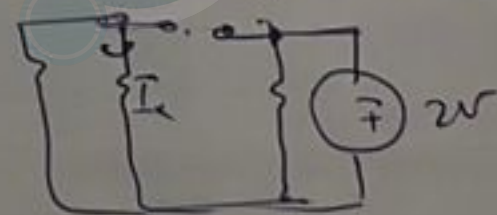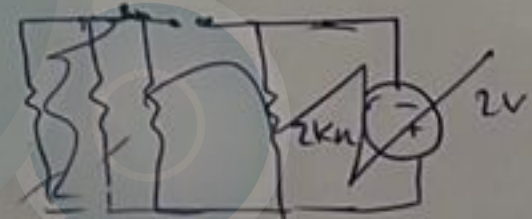


Q15	The current I_x in the given circuit:
a.	-0.33 mA
b.	1.33 mA
c.	-1.33 mA
d.	0 A
e.	0.33 mA




4

$$\frac{1}{2}(C)V^2 =$$

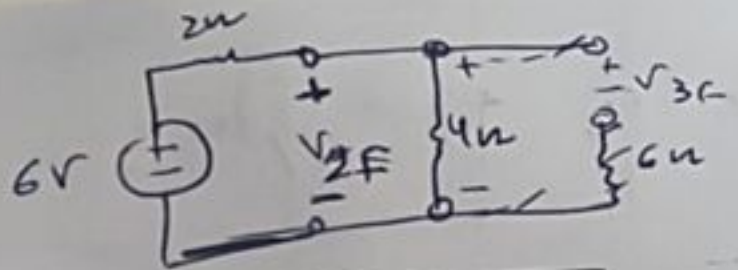


Q6 The energy stored in the 2 F Capacitor is ...

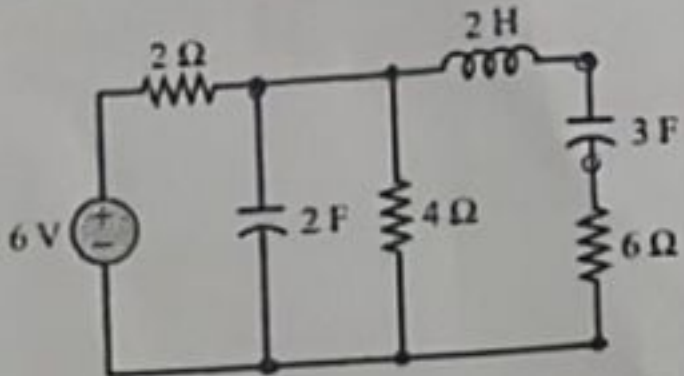- a. 18 J
- b. 24 J
- c. 16 J
- d. 0 J
- e. 6 J




Q7 The equivalent inductance L_T is...

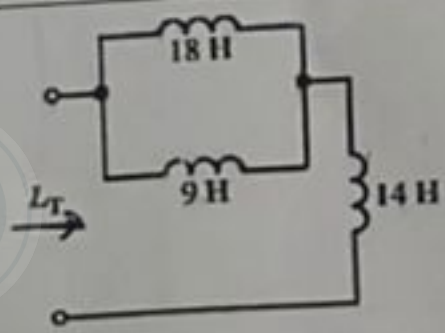- a. 20 H
- b. 9.2 H
- c. 41 H
- d. 27 H
- e. 0 H









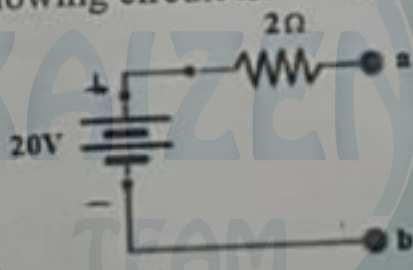
Q8. Norton equivalent circuit to the following circuit is:



$$I_N = \frac{20}{2} = 10 \text{ A}$$

$$R_N = 2\Omega$$

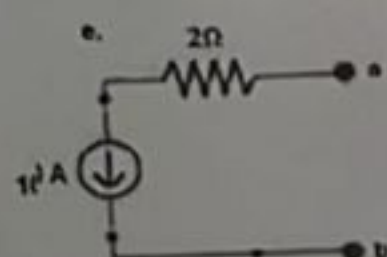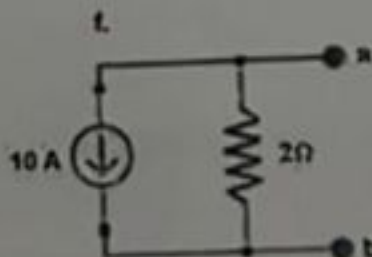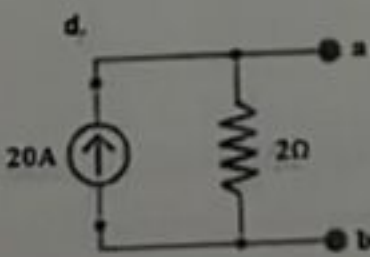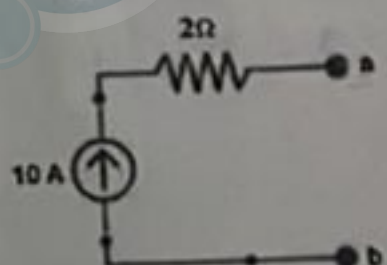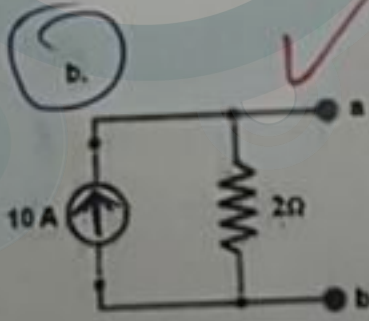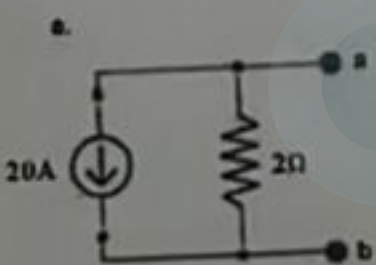

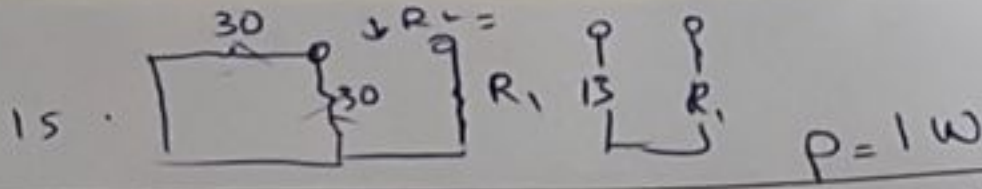


Q1 The maximum transferred power to the load R_L in the following circuit is 1 Watt. This occurs when $R_L = 100\Omega$. Based on the given information, the magnitude of the source voltage V_s is

- a. 20 V
- b. 10 V
- c. 100 V
- ☒ d. 40 V
- e. 1 V

$$\frac{1}{4} \left(\frac{V_{Th}^2}{100} \right) = 1 \times 100 \times 4$$

$$V_{Th} = 20V$$


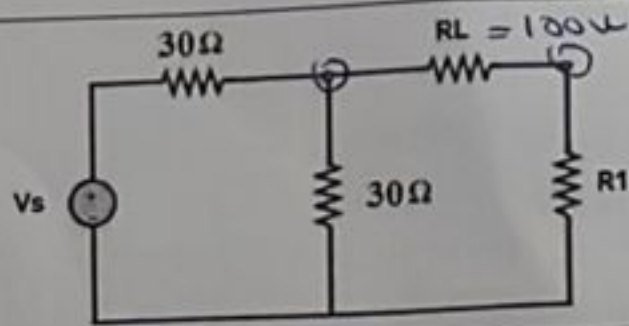


$$R_1 = 85\Omega$$


o vte o

Q2 The maximum transferred power to the load R_L in the following circuit is 1 Watt. This occurs when $R_L = 100\Omega$. Based on the given information, the magnitude of the R_1 is

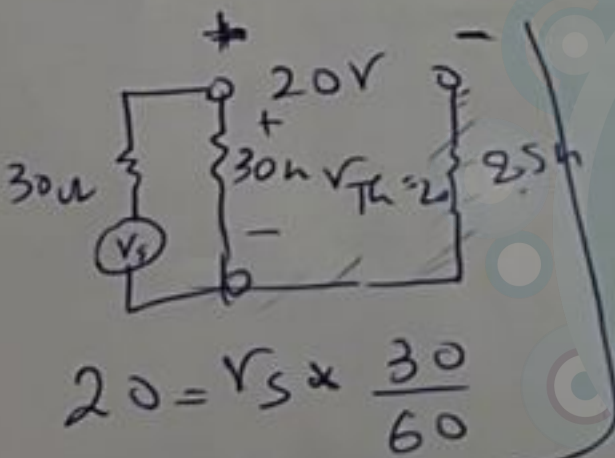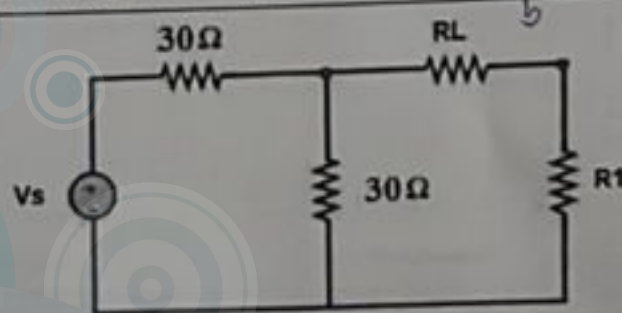
- a. 30 Ω
- b. 60 Ω
- c. 15 Ω
- ☒ d. 85 Ω
- e. 100 Ω



Q3	For the circuit shown below, the current through the inductor i_L is....	
a.	3 A	✓
b.	2 A	
c.	0.5 A	
d.	1 A	
e.	0 A	

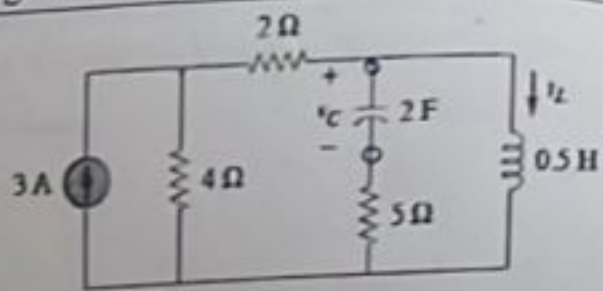

Q4	For the circuit shown below, the voltage across the capacitor v_C is	
a.	6 V	✓
b.	5 V	
c.	30 V	
d.	0 V	
e.	12 V	

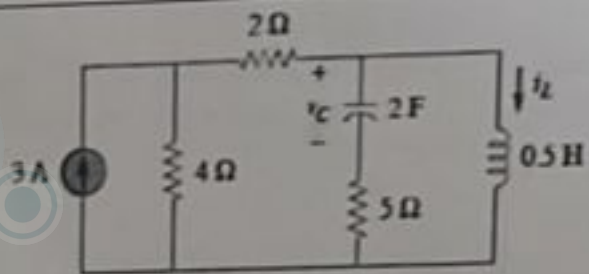

Q5	The equivalent capacitance seen between terminal A-B is...	
a.	5 μF	✓
b.	13.2 μF	
c.	36 μF	
d.	8.72 μF	
e.	4.36 μF	

